

ELEKTRONIKA

Zapiski avditornih vaj

3

EL

Šolsko leto 2009 / 2010
Izvajalec Andrej Žemva

Avtor dokumenta Dominik Peruško
Skeniranje Blaž Potočnik







UREJANJE DOKUMENTA

VERZIJA	01.01
DATUM	13.01.2010





OPOMBE

Bipolarni tranzistor

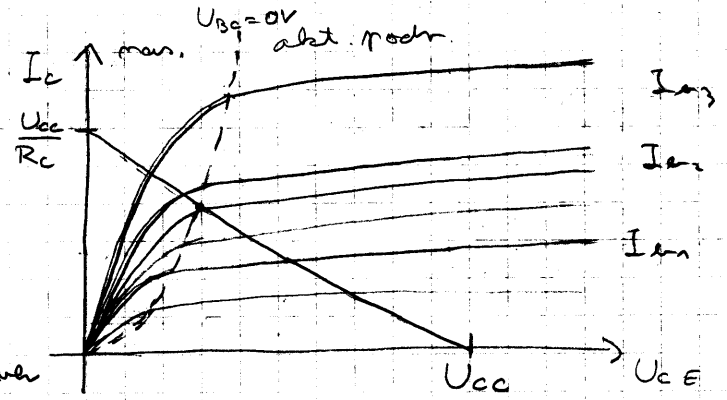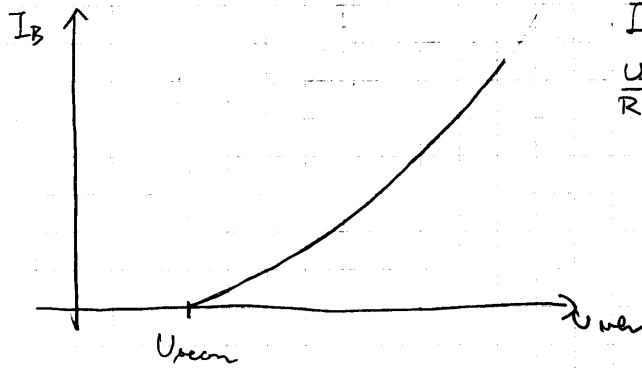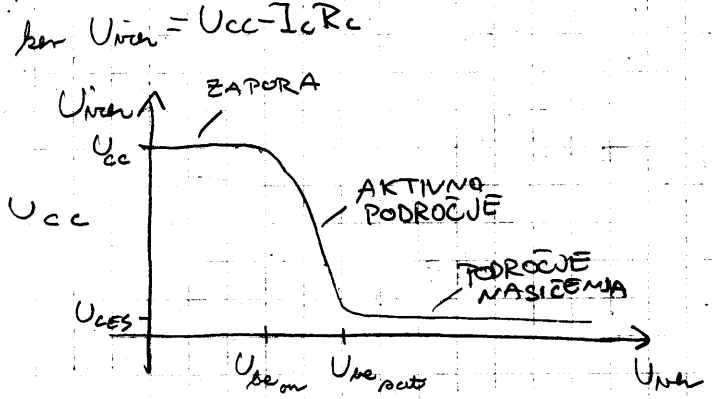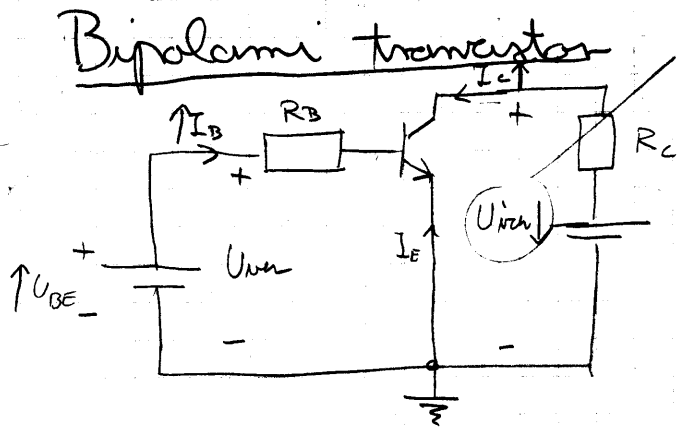

$$U_{cc} = U_{Rc} + U_{CE} = I_c R_c + U_{CE}$$

$$I_c = \frac{U_{cc} - U_{CE}}{R_c}$$

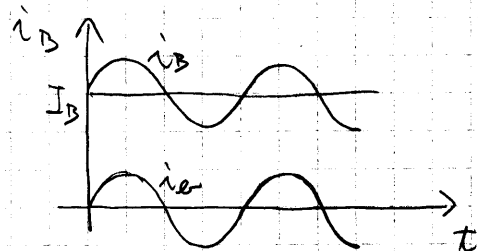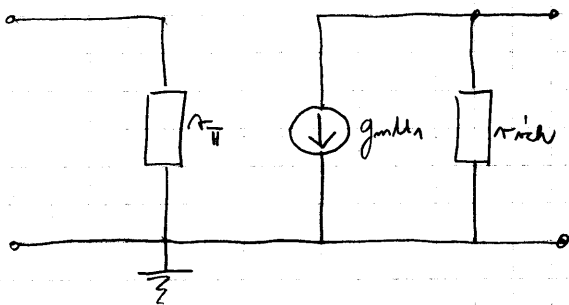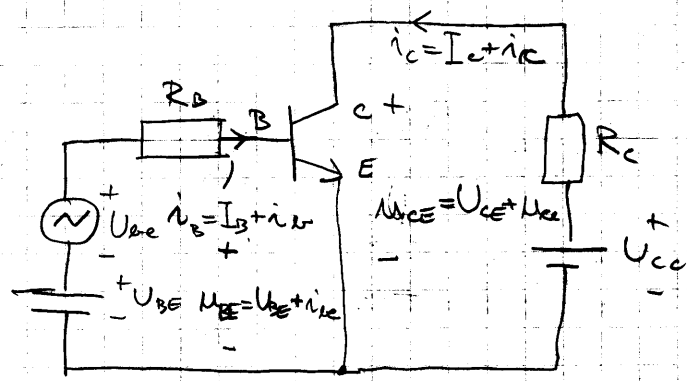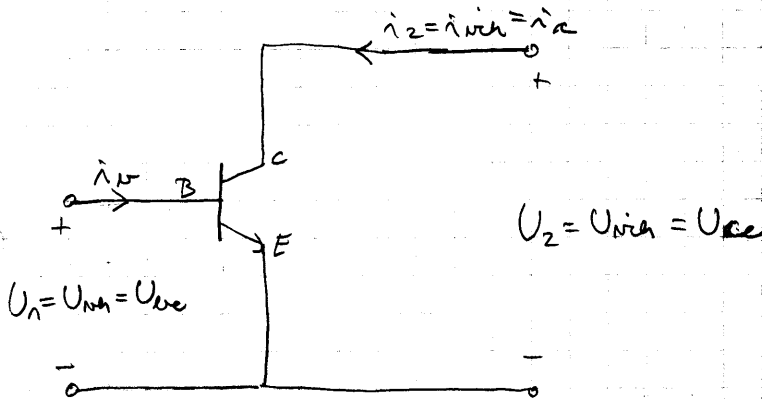

Elementi modello:

$$g_m = \frac{d i_c}{d u_{be}} = \frac{I_s}{U_T} e^{\frac{u_{be}}{U_T}} \Big|_{u_{ce} = U_{BE}} =$$

$$i_c = I_s e^{\frac{u_{be}}{U_T}}$$

$$(g_{21} = \frac{d i_2}{d u_1})$$


$$\rightarrow = \frac{I_s}{U_T} e^{\frac{U_{BE}}{U_T}} = \frac{I_c}{U_T} = \underline{\underline{g_m}}$$

$$r_{\pi} = \frac{d u_{be}}{d i_b} = \frac{d u_{be}}{d i_c} \cdot \beta = \frac{\beta}{g_m} = \underline{\underline{r_{\pi}}}$$

$$(r_{11} = \frac{d u_1}{d i_1})$$

$$i_c = \beta i_b$$


$$i_b = \frac{i_c}{\beta}$$

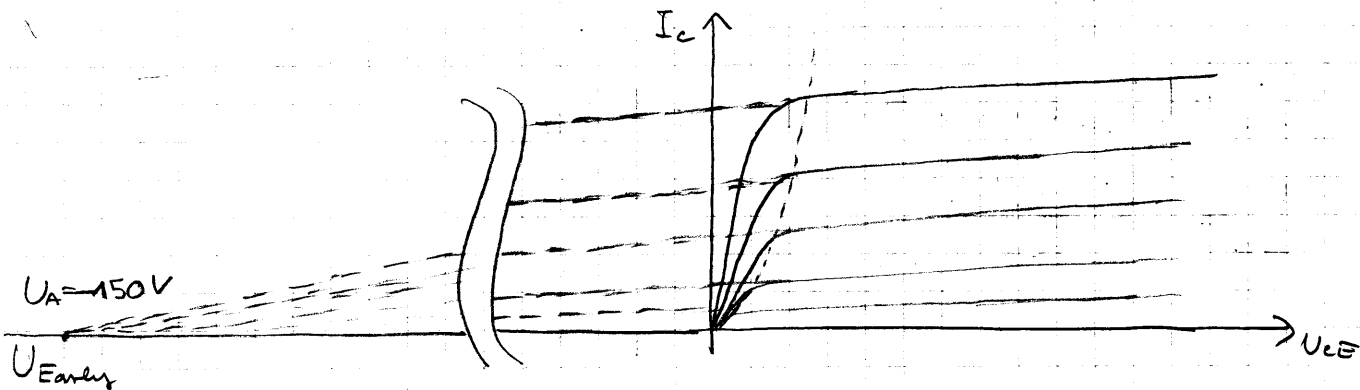


$$\frac{1}{r_{sch}} = \frac{d i_2}{d u_2} = \frac{d i_c}{d u_{CE}} = \frac{I_c}{U_A}$$

$$\underline{\underline{r_{sch} = \frac{U_A}{I_c}}}$$

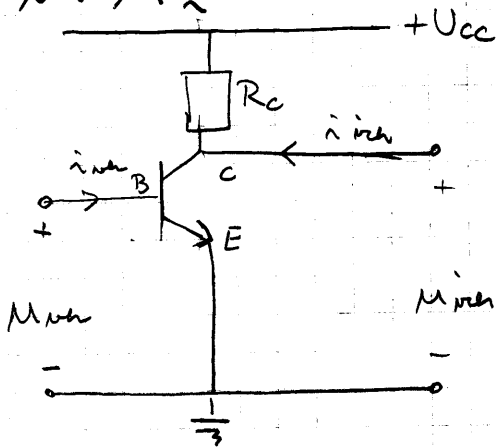Za podano vezje izračunajte r_{vch} , r_{vch} , A_u in A_i



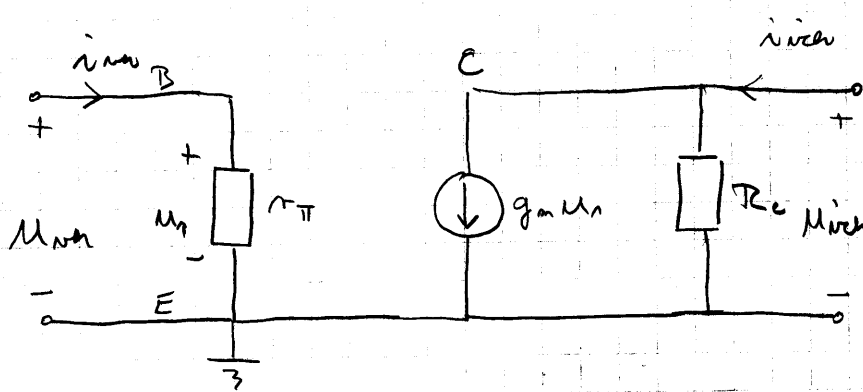$I_c = 100 \mu A$
 $\beta = 100$
 $r_{vch}(\pi) \rightarrow \infty \left(\frac{U_A}{I_c} \right)$
 $R_c = 5 k\Omega$



R_c priklj med C in maso, ker minimumno sprememba napajanja, $\frac{dU_{cc}}{dt} = 0$ - ni U_{cc} -ja

$A_u = \frac{u_{vch}}{u_{vch}}$

$r_{vch} = \frac{u_{vch}}{i_{vch}} = r_{\pi} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_c}{U_T}} = 26 k\Omega$

$r_{vch} = \frac{u_{vch}}{i_{vch}} = R_c = 5 k\Omega$

obhod kratko sklenemo, tak, vir odpade


$A_u = \frac{u_{vch}}{u_{vch}} = \frac{-g_m u_{\pi} R_c}{u_{\pi}} = -g_m R_c = -\frac{I_c}{U_T} R_c =$

$u_{vch} = u_{RC} = -g_m u_{\pi} R_c = -19,2$


$A_i = \frac{i_{vch}}{i_{vch}} = \frac{i_c}{i_b} = \frac{\beta i_b}{i_b} = \beta = 100$

$i_{vch} = g_m u_{\pi} = g_m I_{vch} r_{\pi} \Rightarrow A_i = g_m r_{\pi} = g_m \frac{\beta}{g_m} = \beta$

Za podano vezje izračunajte A_u

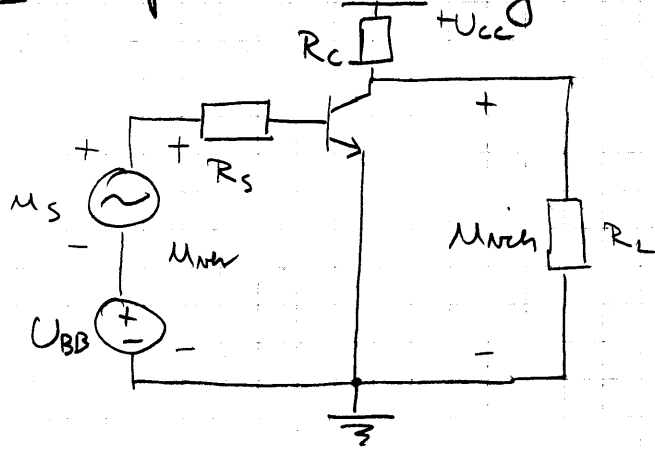
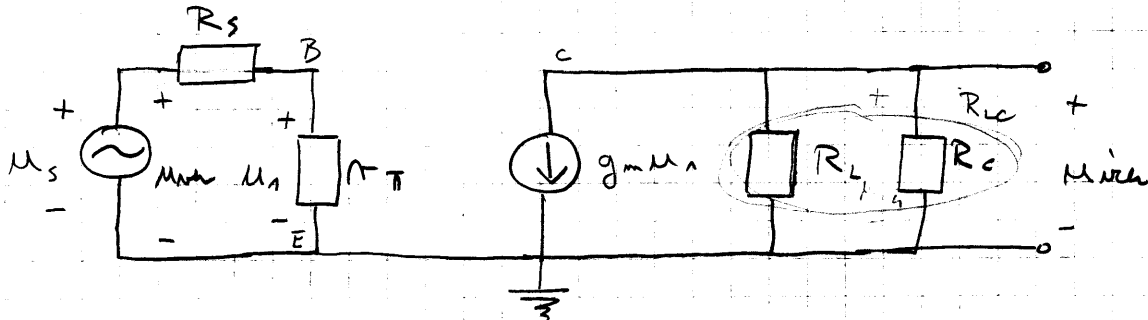
$$\begin{aligned} \beta &= 100 \\ I_c &= 100 \mu\text{A} \\ R_C &= 5 \text{ k}\Omega \\ R_S &= 20 \text{ k}\Omega \\ R_L &= 10 \text{ k}\Omega \end{aligned}$$



$$A_u = \frac{u_{vch}}{u_{vch}}$$

$$\frac{1}{R_{Lc}} = \frac{1}{R_L} + \frac{1}{R_C} \Rightarrow R_{Lc} = \frac{R_L R_C}{R_L + R_C}$$

$$u_{vch} = -g_m u_1 \frac{R_L R_C}{R_L + R_C} = -g_m \frac{R_L R_C}{R_S + r_{\pi}} u_{vch} \frac{R_L R_C}{R_L + R_C}$$


~~$$A_u = -g_m \frac{R_L R_C}{R_L + R_C}$$~~

$$u_1 = \frac{r_{\pi}}{R_S + r_{\pi}} u_{vch}$$

~~$$A_u = \frac{u_{vch}}{u_{vch}} = -g_m \frac{r_{\pi}}{R_S + r_{\pi}} \frac{R_L R_C}{R_L + R_C} = -4,25$$~~

▣ Vračunajte delovno točko in porabo moči na tranzistorju

Del. točka: I_c , U_{CE}

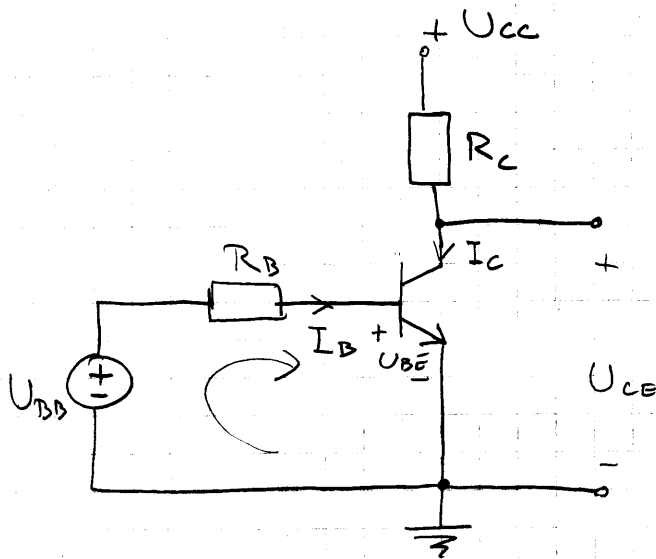

$$U_{CC} = 10V$$

$$U_{BB} = 4V$$

$$R_C = 2k\Omega$$

$$R_B = 220k\Omega$$

$$U_{BE} = 0,7V$$

$$\beta = 200$$

$$I_c = \beta I_B$$

$$-U_{BB} + R_B I_B + U_{BE} = 0$$

$$I_B = \frac{U_{BB} - U_{BE}}{R_B} = 15\mu A$$

$$I_c = \beta I_B = \underline{\underline{3mA}}$$

$$U_{CE} = U_{CC} - I_c R_C = \underline{\underline{4V}}$$


Akt. področje: $I_c = \beta I_B$
 $U_{CE} \gg U_{CES}$

$$P_T = I_B U_{BE} + I_c U_{CE} = 15\mu A \cdot 0,7V + 3mA \cdot 4V =$$

$$= 0,0105mW + 12mW = 12,0105mW \approx 12mW$$

($I_c U_{CE}$)

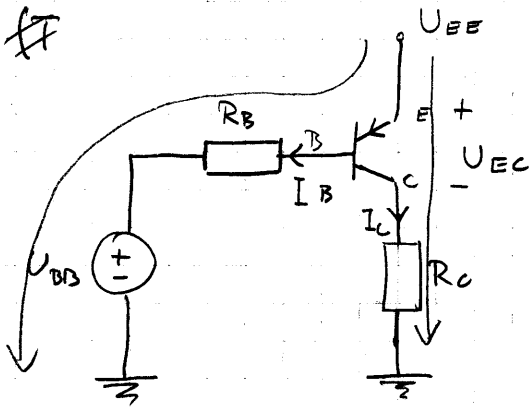▣ Iračunajte I_B, I_C, I_E in R_C tako, da bo $U_{EC} = \frac{1}{2} U_{EE}$



$$U_{EE} = 5V$$

$$U_{BB} = 1,5V$$

$$R_B = 580k\Omega$$

$$U_{EB} = 0,6V$$

$$\beta = 100$$

$$U_{EC} = 2,5V \Rightarrow U_{RC} = 2,5V (= U_{EE} - U_{EC})$$


$$U_{EE} = U_{BB} + R_B I_B + U_{EB} \Rightarrow I_B = \frac{U_{EE} - U_{BB} - U_{EB}}{R_B} = 5\mu A$$

$$I_C = \beta \cdot I_B = 0,5mA$$

$$I_E = I_B + I_C = 0,505mA$$

$$R_C = \frac{U_{RC}}{I_C} = 5k\Omega$$

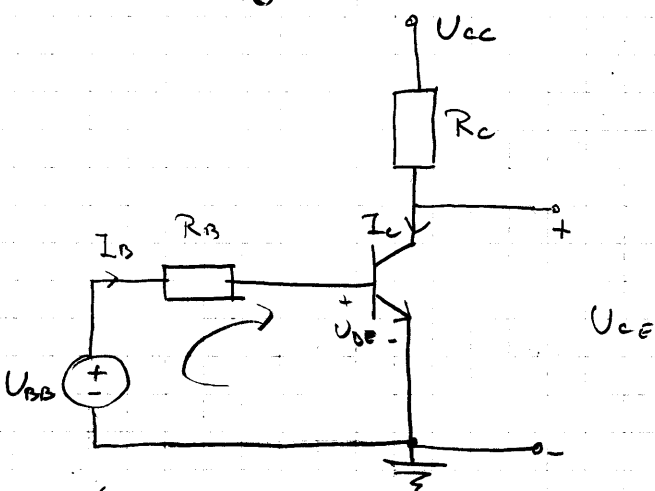▣ Iračunajte del. točko in moč na tranzistorju



$$U_{CC} = 10V$$

$$U_{BB} = 8V$$

$$R_C = 4k\Omega$$

$$R_B = 220k\Omega$$

$$\beta = 100$$

$$U_{BE} = 0,7V$$

$$U_{CES} = 0,2V$$

$$-U_{BB} + R_B I_B + U_{BE} = 0$$

$$I_B = \frac{U_{BB} - U_{BE}}{R_B} = 33,2 \mu\text{A}$$

$$\text{Akt. podr.}: I_C = \beta I_B = 3,32 \text{mA}$$

$$U_{CE} = U_{CC} - R_C I_C = -3,28 \text{V} // \text{transistor ni v akt. podr.}$$

Področje nasičenja

$$I_C = \beta \cdot I_B //$$

$$U_{CE} = U_{CES}$$

$$I_C = - \frac{U_{CES} - U_{CC}}{R_C} = \frac{U_{CC} - U_{CES}}{R_C} = 2,45 \text{mA}$$


$$\frac{I_C}{I_B} = 74 < \beta$$

nasičenje	akt. področje
$I_C < \beta I_B$	$I_C = \beta I_B$
$U_{CE} = U_{CES}$	$U_{CE} > U_{CES}$
$U_{BC} > 0$	$U_{BC} < 0$

$$\begin{aligned}
 P &= I_B U_{BE} + I_C U_{CES} = 0,0332 \text{mA} \cdot 0,7 \text{V} + 2,45 \text{mA} \cdot 0,2 \text{V} \\
 &= 0,023 \text{mW} + 0,49 \text{mW} \\
 &= 0,513 \text{mW}
 \end{aligned}$$

☑ Za podano vezje določite menomo karakt

$$U_{\text{vch}} = f(U_{\text{vni}})$$

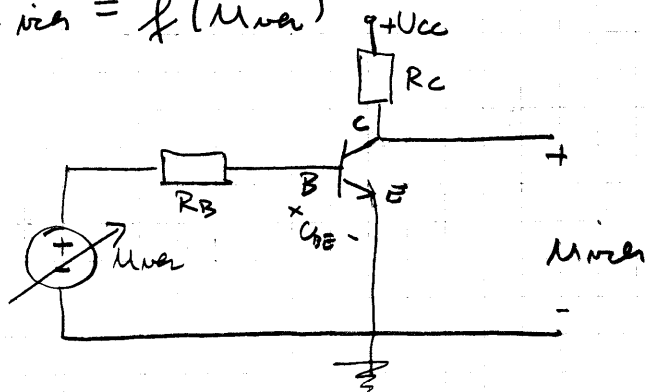

transistori rajni, $U_{\text{vni}} < U_{\text{BE}}$

$$U_{\text{cc}} = 5\text{V}$$


$$R_C = 5\text{k}\Omega$$

$$R_B = 150\text{k}\Omega$$

$$U_{\text{BE}} = 0,7\text{V}$$

$$\beta = 120$$

$$U_{\text{CES}} = 0,2\text{V}$$

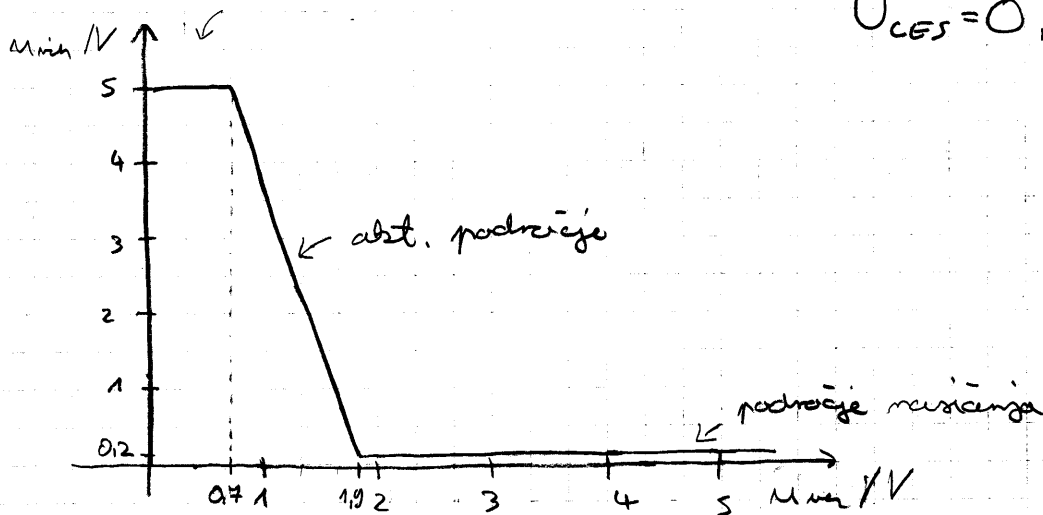

$$U_{\text{vch}} = U_{\text{cc}} - U_{\text{rc}} = U_{\text{cc}} - I_C R_C = U_{\text{cc}} - \beta I_B R_C$$

$$I_B = \frac{U_{\text{vni}} - U_{\text{BE}}}{R_B}$$

$$U_{\text{vch}} = U_{\text{cc}} - \beta R_C \frac{U_{\text{vni}} - U_{\text{BE}}}{R_B}$$

$$U_{\text{vni}} = 0,7 \Rightarrow U_{\text{vch}} = U_{\text{cc}}$$

$$U_{\text{vch}} = 0,2\text{V} \Rightarrow R_B U_{\text{vch}} = R_B U_{\text{cc}} - \beta R_C U_{\text{vni}} + \beta R_C U_{\text{BE}}$$



$$U_{\text{vni}} = \frac{R_B U_{\text{vch}} - R_B U_{\text{cc}} - \beta R_C U_{\text{BE}}}{-\beta R_C}$$

$$U_{\text{vni}} = \frac{R_B (U_{\text{cc}} - U_{\text{vch}}) + \beta R_C U_{\text{BE}}}{\beta R_C}$$


$$= \frac{R_B (U_{\text{cc}} - U_{\text{vch}})}{\beta R_C} + U_{\text{BE}}$$

$$= \frac{150 (5 - 0,2)}{120 \cdot 5} + 0,7 = 1,9\text{V}$$

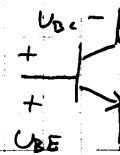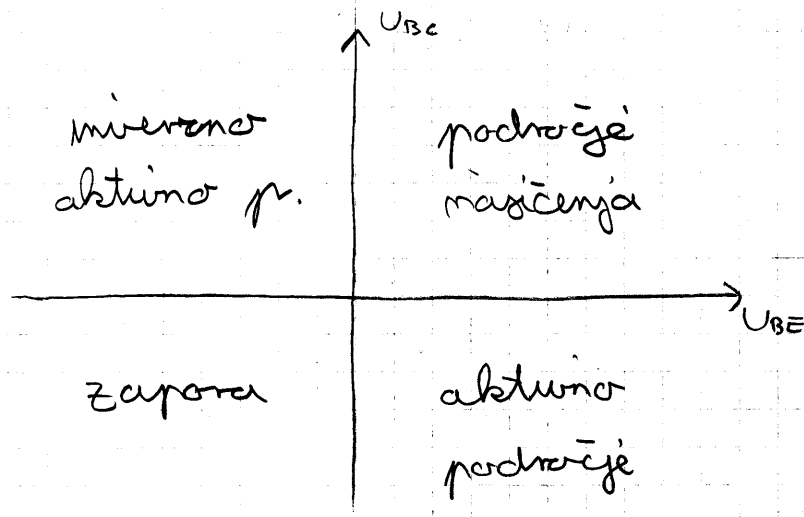
$$A_u = \frac{d u_{\text{Mira}}}{d u_{\text{Mna}}} = \frac{5V - 0,2V}{0,7V - 1,9V} = -4$$



Primer: karakterist. rač. pnp

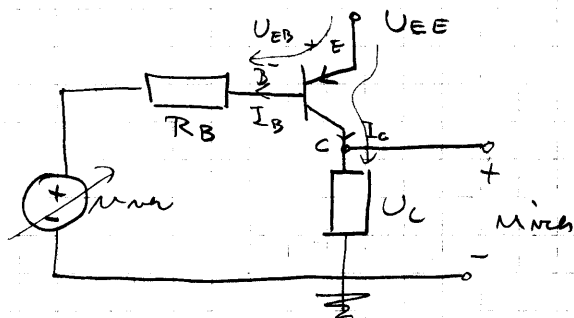

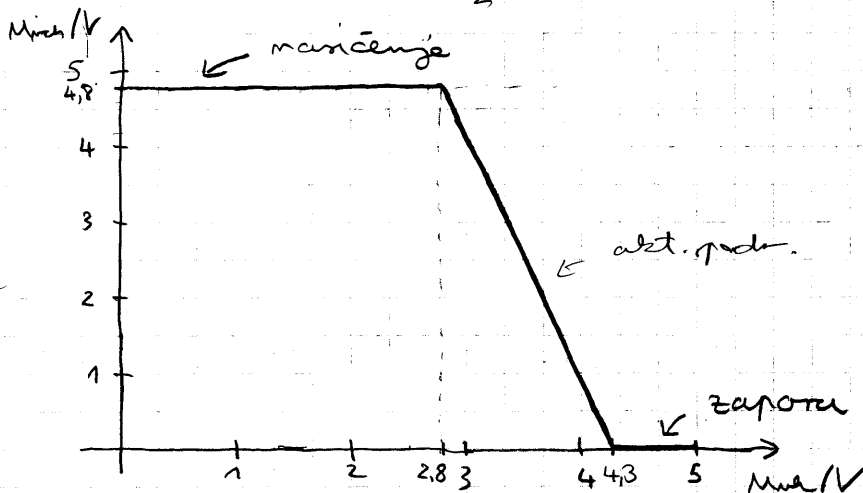- $U_{EB} = 0,7V$
- $U_{EE} = 5V$
- $\beta = 80$
- $U_{EC} = 0,2V$
- $R_C = 8k\Omega$
- $R_B = 200k\Omega$



$$U_{\text{Mira}} = U_{EE} I_c R_c$$

$$= \beta I_B R_c$$

$$= \frac{R_c}{R_B} \beta (U_{EE} - U_{EB} - U_{Mna})$$

$$U_{EE} = U_{EB} + U_{Mna} + R_B I_B$$

$$I_B = \frac{U_{EE} - U_{EB} - U_{Mna}}{R_B}$$


$$4,7 = \frac{1}{80} \cdot \frac{200}{8} \cdot 4,8$$

$$U_{Mna} = -\frac{1}{\beta} \frac{R_B}{R_c} U_{\text{Mira}} + U_{EE} - U_{EB} = U_{EE} - U_{EB} - \frac{1}{\beta} \frac{R_B}{R_c} U_{\text{Mira}}$$

$$4,7 = \frac{200}{80} \cdot \frac{4,8}{8} + 5 - 0,7 - \frac{1}{80} \cdot \frac{200}{8} U_{\text{Mira}}$$

$$U_{\text{Mira}} = 4,8V \rightarrow U_{Mna} = 2,8V$$

Za podano vezje izračunajte D.T.

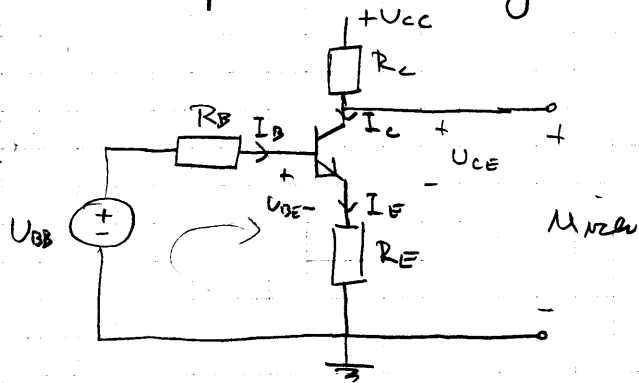

$$U_{CC} = 12V$$

$$U_{BB} = 6V$$

$$R_C = 0,4 k\Omega$$

$$R_B = 25 k\Omega$$

$$R_E = 0,6 k\Omega$$

$$U_{BE} = 0,7V$$

$$\beta = 75$$

$$-U_{BB} + R_B I_B + U_{BE} + R_E I_E = 0$$

$$-U_{CC} + R_C I_C + U_{CE} + R_E I_E = 0$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

$$-U_{BB} + R_B I_B + U_{BE} + R_E \beta I_B + R_E I_B = 0$$

$$-U_{CC} + R_C \beta I_B + U_{CE} + R_E \beta I_B + R_E I_B = 0$$


$$-U_{BB} + R_B I_B + R_E (1 + \beta) I_B = U_{BB} - U_{BE}$$

$$I_B = \frac{U_{BB} - U_{BE}}{R_B + R_E (1 + \beta)} = 75,1 \mu A$$

$$I_C = \beta I_B = 5,63 mA$$



$$U_{CE} = U_{CC} - I_C (R_C + R_E (\beta + 1)) = 6,32V$$

meriti
stevilj

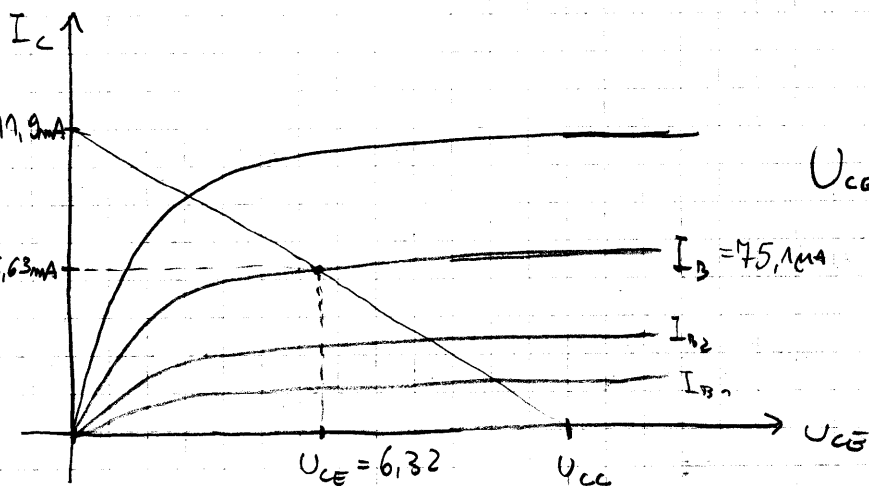

$$I_E = \frac{\beta + 1}{\beta} I_C$$
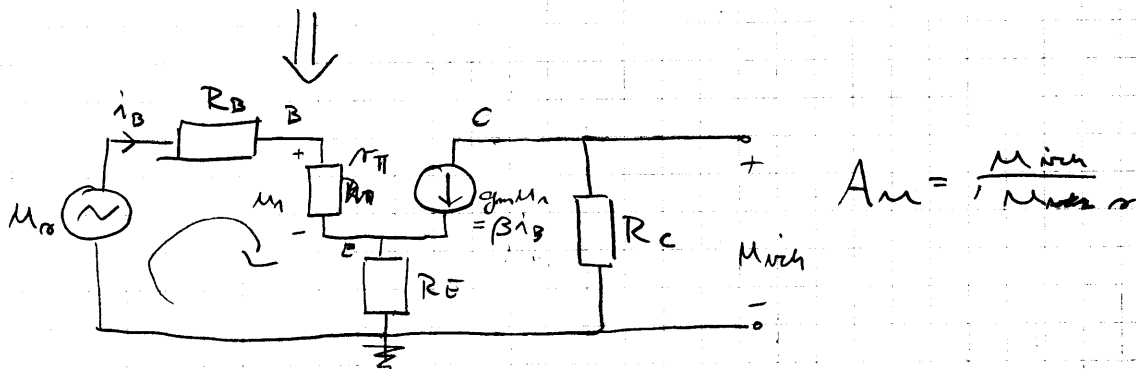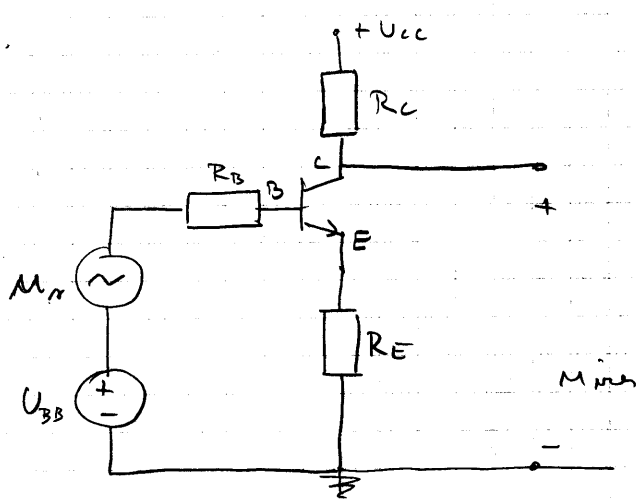
$$U_{CE} = U_{CC} - I_C R_C - \frac{\beta + 1}{\beta} I_C R_E = U_{CC} - I_C \left[R_C + \frac{\beta + 1}{\beta} R_E \right] = U_{CC} - I_C \cdot 1,01 k\Omega$$



$$A_u = \frac{U_{Misch}}{U_{\alpha}}$$

$$\begin{aligned} U_{Misch} &= U_{Rc} \\ &= -g_m u_{\alpha} R_c \\ &= -\beta i_B R_c \end{aligned}$$

$$\begin{aligned} u_{\alpha} &= R_B i_B + r_{\pi} i_B + R_E (i_B + \beta i_B) \\ &= i_B (R_B + r_{\pi} + R_E (1 + \beta)) \end{aligned}$$

$$i_B = \frac{u_{\alpha}}{R_B + r_{\pi} + R_E (1 + \beta)}$$

$$U_{Misch} = -\frac{\beta R_c}{R_B + r_{\pi} + R_E (1 + \beta)} u_{\alpha}$$

$$A_u = -\frac{\beta R_c}{R_B + r_{\pi} + R_E (1 + \beta)} = -\frac{R_c}{\frac{R_B}{\beta} + \frac{1}{g_m} + \frac{1 + \beta}{\beta} R_E}$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta \cdot U_T}{I_c}$$

$$\frac{r_{\pi}}{\beta} = \frac{1}{g_m}$$

$$g_m = \frac{I_c}{U_T} = \frac{5,63 \text{ mA}}{26 \text{ mV}}$$

$$\frac{1}{g_m} = \frac{26 \text{ mV}}{5,63 \text{ mA}}$$

$$A_u = -0,42$$

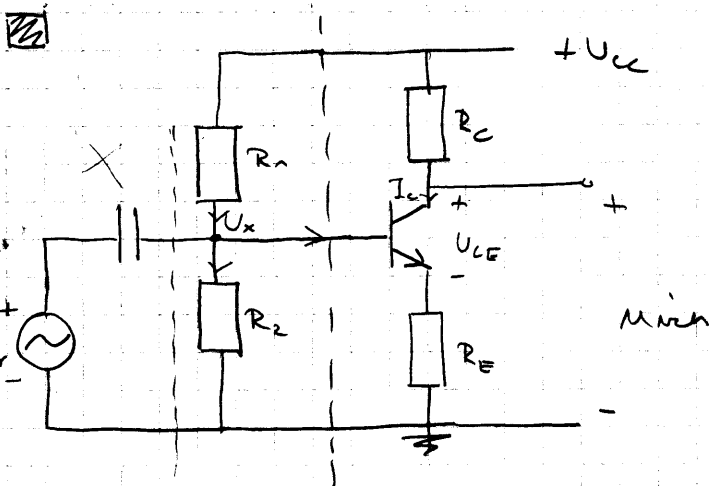

Iteracijske D.T.!

$$R_1 = 56 \text{ k}\Omega$$

$$R_2 = 12,2 \text{ k}\Omega$$

$$R_C = 2 \text{ k}\Omega$$

$$R_E = 0,4 \text{ k}\Omega$$

$$U_{CC} = 10 \text{ V}$$

$$U_{BE} = 0,7 \text{ V}$$

$$\beta = 100$$

$$I_{R_1} = I_{R_2} + I_B$$


$$\frac{U_{CC} - U_x}{R_1} = \frac{U_x}{R_2} + I_B \quad (1)$$

$$U_x = U_{RE} + U_{BE}$$

$$U_x = (1 + \beta) I_B R_E + U_{BE} \quad (2)$$

Iz (1) in (2) bi ~~izračunati~~ ^{izračunati} U_x in I_B .

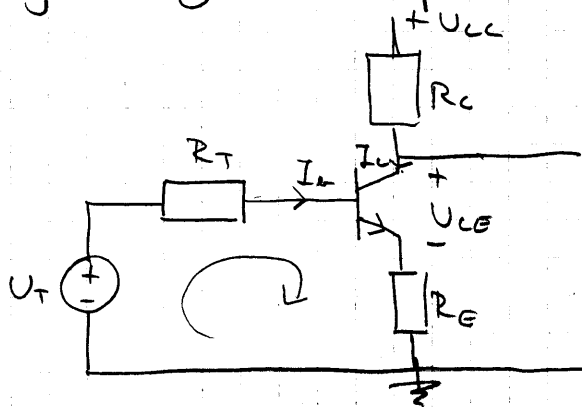Bolj elegantna pot: Theveninova transform.



$$U_T = \frac{R_2}{R_1 + R_2} U_{CC} = 1,79 \text{ V}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = 10 \text{ k}\Omega$$


$$U_T = R_T I_B + U_{BE} + (1 + \beta) I_B R_E \Rightarrow I_B = \frac{U_T - U_{BE}}{R_T + (1 + \beta) R_E} = 21,6 \mu\text{A}$$

$$I_C = \beta I_B = 2,16 \text{ mA}$$

$$U_{CE} = U_{CC} - R_C I_C - R_E I_E =$$

$$= U_{CC} - R_C I_C - R_E (I_C + I_B) = \underline{\underline{4,81V}}$$

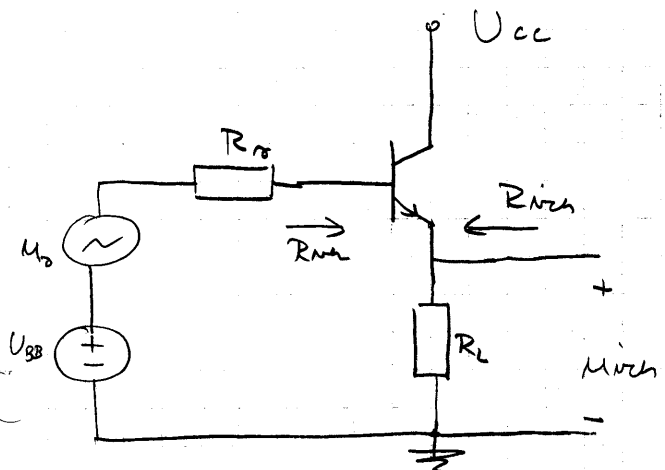Za podana vezje izračunajte R_{in} , R_{iB} in A_u




$$\beta = 100$$

$$I_C = 100 \mu A \Rightarrow r_{\pi} = 26 k\Omega$$

$$R_S = 1 k\Omega$$

$$R_L = 1 k\Omega$$

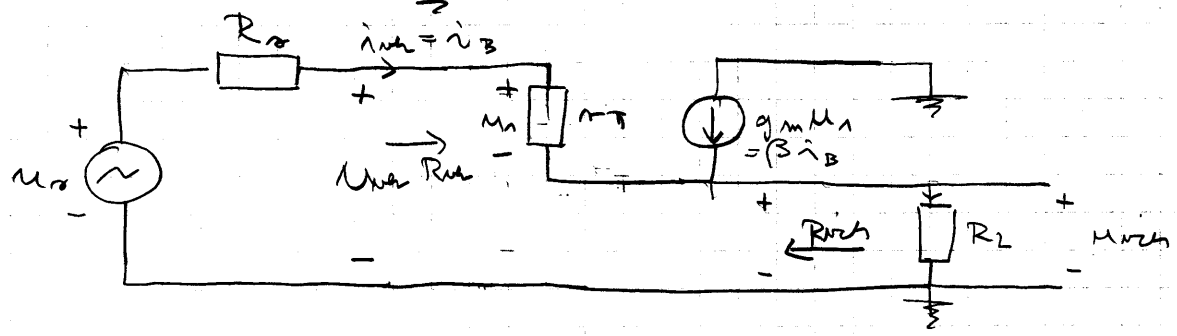

$$A_u = \frac{u_{ich}}{u_B}$$

$$i_B + g_m u_{be} = i_{R_L}$$

$$\frac{u_B - u_{ich}}{R_S + r_{\pi}} + \beta \frac{u_B - u_{ich}}{R_S + r_{\pi}} = \frac{u_{ich}}{R_L}$$


$$\frac{u_B (1 + \beta)}{R_S + r_{\pi}} = \frac{u_{ich} (1 + \beta)}{R_S + r_{\pi}} + \frac{u_{ich}}{R_L} = \frac{u_{ich} [(1 + \beta) R_L + R_S + r_{\pi}]}{(R_S + r_{\pi}) R_L}$$

$$u_B = \frac{(1 + \beta) R_L + R_S + r_{\pi}}{(1 + \beta) R_L} u_{ich}$$

$\underbrace{\hspace{10em}}_{1/A_u}$

$A_{u_{id}}$

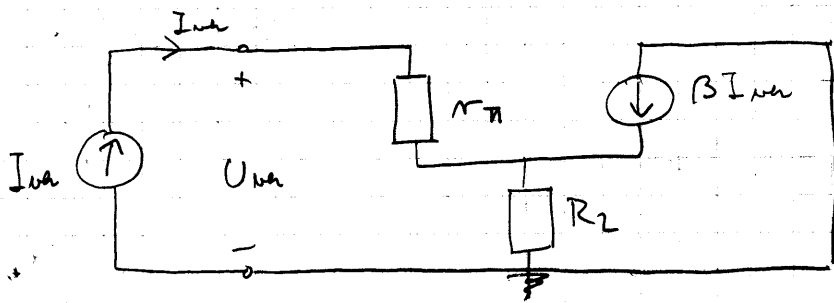
$$A_u = \frac{1}{1 + \frac{R_S + r_{\pi}}{(1 + \beta) R_L}} = 0,79$$



$$R_{ua} = \frac{U_{ua}}{I_{ua}}$$

$$U_{ua} = U_{r_{\pi}} + U_{R_L} = r_{\pi} I_{ua} + R_L (I_{ua} + \beta I_{ua})$$
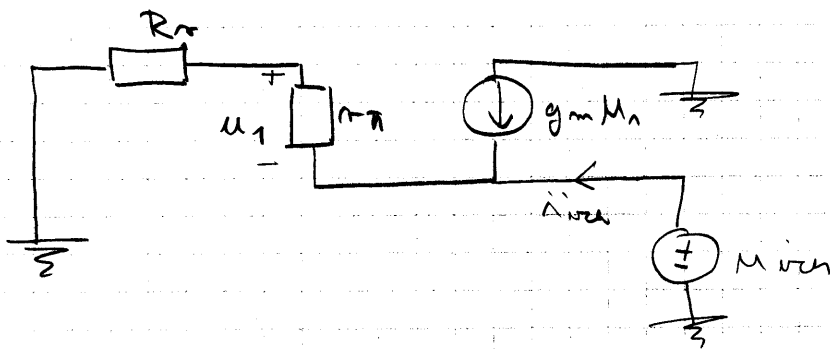
$$R_{ua} = r_{\pi} + R_L (1 + \beta) = 127 \text{ k}\Omega$$



R_{ich} gledamo pri kratkosplojenem izhodni vhodni




$$R_{ich} = \frac{U_{ich}}{I_{ich}}$$

$$U_1 = -\frac{r_{\pi}}{r_{\pi} + R_s} U_{ich}$$

$$I_{ich} = -g_m U_1 + \frac{U_{ich}}{r_{\pi} + R_s} = \left(g_m \frac{r_{\pi}}{r_{\pi} + R_s} + \frac{1}{r_{\pi} + R_s} \right) U_{ich} = \frac{g_m r_{\pi} + 1}{r_{\pi} + R_s} U_{ich} = \frac{\beta + 1}{r_{\pi} + R_s} U_{ich}$$

$$R_{ich} = \frac{r_{\pi} + R_s}{\beta + 1} - \text{niska izhodna upornost} = 270 \Omega$$

16

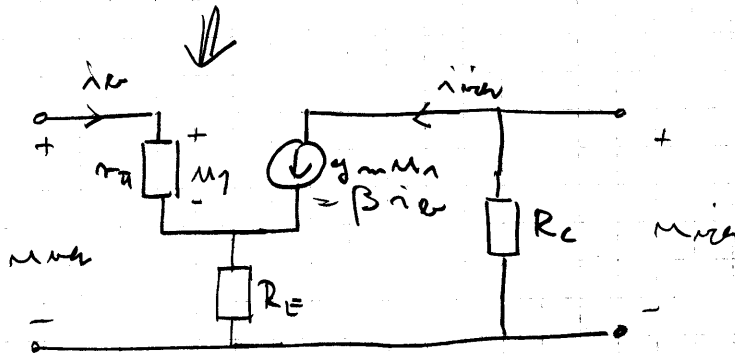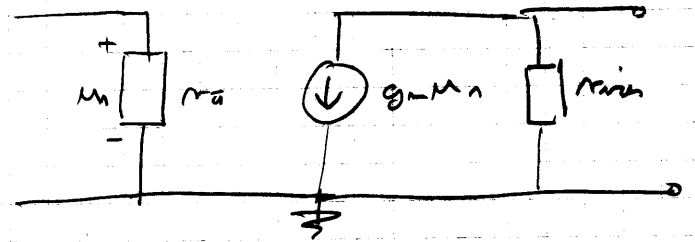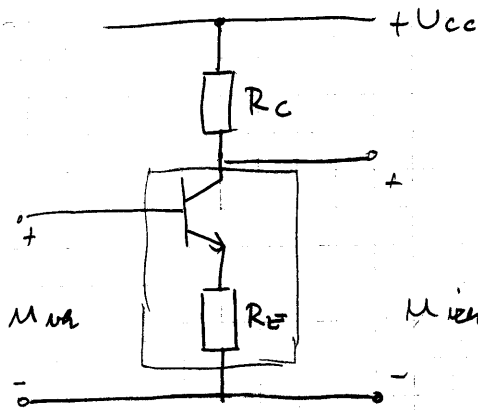

$$\begin{aligned}
 u_{out} &= u_{Rc} + u_{RE} \\
 &= i_{test} R_c + (1 + \beta) i_{test} R_E \\
 &= i_{test} (R_c + (1 + \beta) R_E)
 \end{aligned}$$



$$R_{in} = \frac{u_{in}}{i_{test}} = R_c + (1 + \beta) R_E = r_{\pi} + (1 + \frac{\beta}{r_{\pi}}) R_E = \underline{\underline{r_{\pi} (1 + g_m R_E)}}$$

$$\begin{aligned}
 u_{out} &= u_{Rc} + u_{RE} \\
 &= i_c R_c + (i_c + i_e) R_E \\
 &= \frac{i_c}{\beta} R_c + (\frac{1}{\beta} + 1) i_c R_E \\
 &= i_c \left[\frac{1}{\beta} R_c + (\frac{1}{\beta} + 1) R_E \right]
 \end{aligned}$$


$$g_m \rightarrow \frac{r_{\pi}}{\beta} = \frac{1}{g_m}$$

$$g_m' = \frac{i_c}{u_{in}} = \frac{1}{\frac{1}{g_m} + R_E (1 + \frac{1}{\beta})} = \underline{\underline{\frac{g_m}{1 + g_m R_E}}}$$

$$r_{out}' = r_{out} (1 + g_m R_E)$$

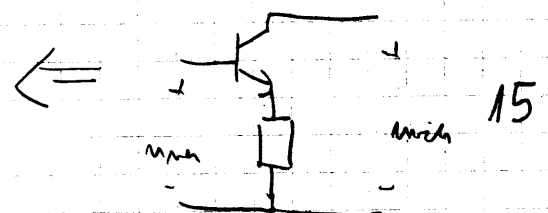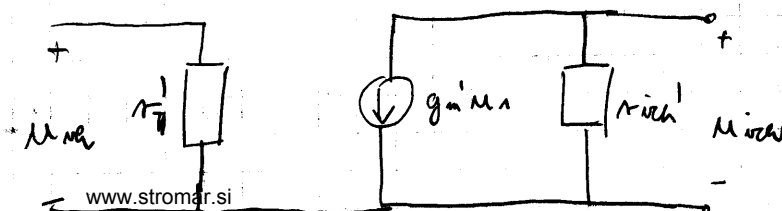

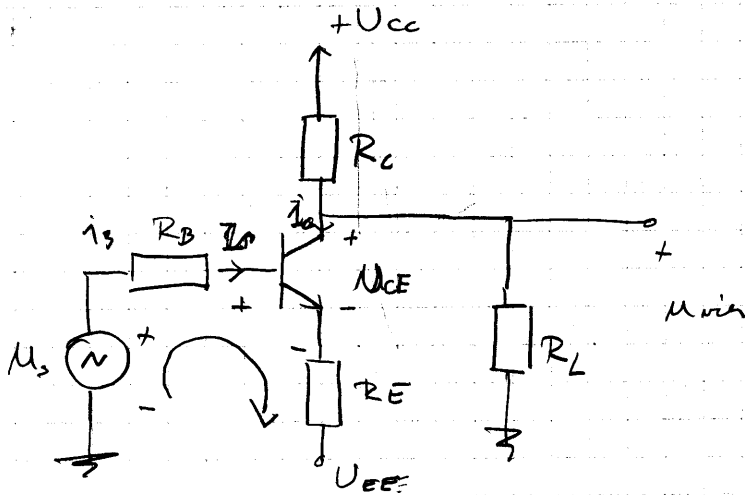▣ Iščite delovno točko in delovno premico za podano vezje



- $U_{CC} = 12V$
- $U_{EE} = -5V$
- $R_C = R_L = R_E = 5k\Omega$
- $R_B = 10k\Omega$
- $U_{BE} = 0,7V$
- $\beta = 100$

$$I_B R_B + U_{BE} + R_E I_E \stackrel{U_{EE}}{=} 0$$

$$I_B R_B + U_{BE} + R_E I_B (\beta + 1) \stackrel{U_{EE}}{=} 0$$

$$I_B = \frac{-U_{BE} - U_{EE}}{R_B + R_E(\beta + 1)} = 8,35 \mu A$$

$$I_C = \beta I_B = \underline{\underline{0,835 mA}}$$

$$I_C = I_{RC} - I_{RL}$$

$$I_{RC} = \frac{U_{RC}}{R_C} = \frac{U_{CC} - U_{vish}}{R_C}$$


$$I_C = \frac{U_{CC} - U_{vish}}{R_C} - \frac{U_{vish}}{R_L}$$

$$U_{vish} = 3,91V$$

$$U_{CE} = U_{vish} - U_{RE} - U_{EE}$$

$$U_{CE} = U_{vish} - I_E R_E - U_{EE} = \underline{\underline{4,7V}} \quad \checkmark \text{ akt. obm.}$$

Ojačanje R_B

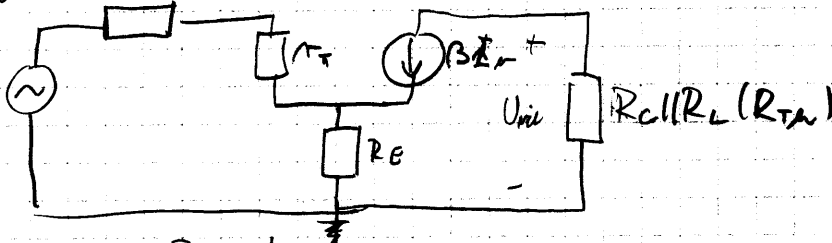

$$U_{vish} = -\beta I_E R_{th}$$

$$R_{th}$$

$$U_0 = U_{RB} + U_{r_{BE}} + U_{RE} \quad 1b$$

$$= I_B R_B + I_B r_{BE} + (1 + \beta) R_E I_B$$


$$I_B = \frac{U_0}{R_B + r_{BE} + (1 + \beta) R_E}$$

$$U_{vish} = -\beta \frac{R_{th} U_0}{R_B + r_{BE} + (1 + \beta) R_E}$$

$$A_M = -\frac{\beta R_{th}}{R_B + r_{BE} + (1 + \beta) R_E}$$

Delovna točka:

ELN, 12.11

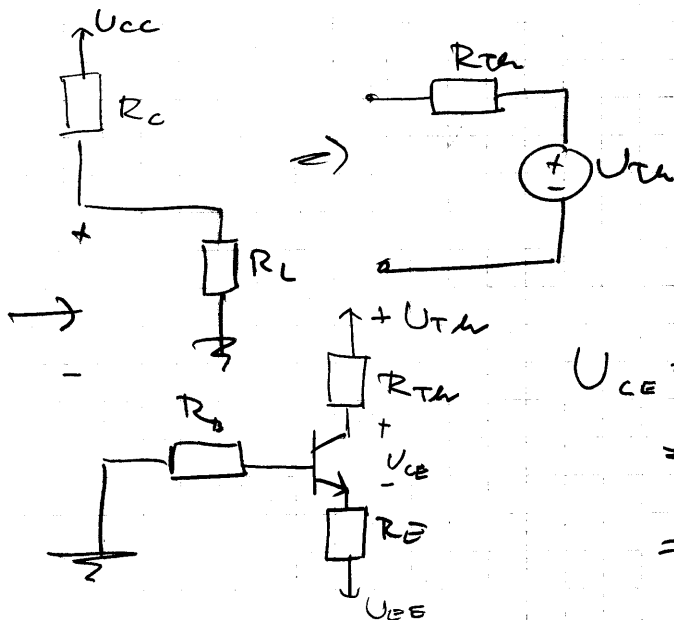

$$R_{TH} = R_c \parallel R_L = 2,5 k\Omega$$


$$U_{TH} = \frac{R_L}{R_c + R_L} \cdot U_{CC} = 6V$$

$$U_{CE} = U_{TH} - U_{EE} - U_{R_{TH}} - U_{R_E}$$

$$= U_{TH} - U_{EE} - I_C R_{TH} - I_E R_E$$


$$= 6V - 5V - I_C \cdot 2,5 k\Omega - \frac{101}{100} I_C \cdot 5 k\Omega$$

$$U_{CE} = 1V - I_C \cdot 7,55 k\Omega$$

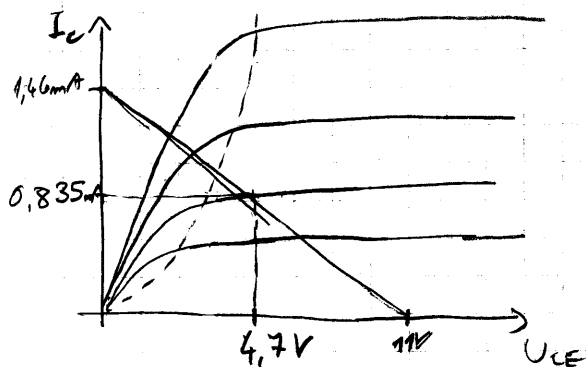

▣ Iračunajte R_B in R_C za dane zahteve!

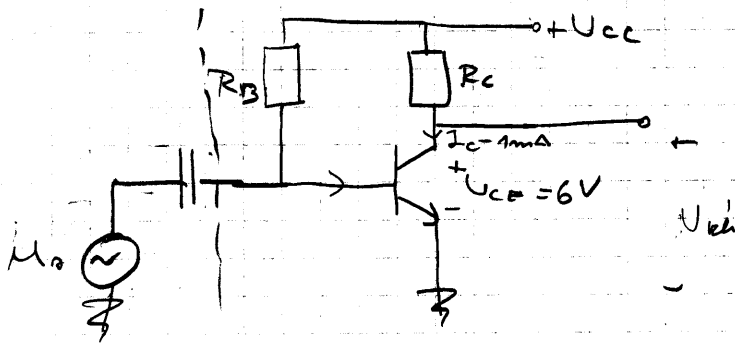- $I_C = 1 mA$
- $U_{CE} = 6V$
- $U_{BE} = 0,7V$
- $U_{CC} = 12V$
- $\beta = 100$




$$U_{CC} = R_C I_C + U_{CE} \Rightarrow R_C = \frac{U_{CC} - U_{CE}}{I_C} = 6 k\Omega$$


$$I_B = \frac{I_C}{\beta} = \frac{1 mA}{100} = 10 \mu A$$

$$R_B = \frac{U_{CC} - U_{BE}}{I_B} = 1,13 M\Omega$$

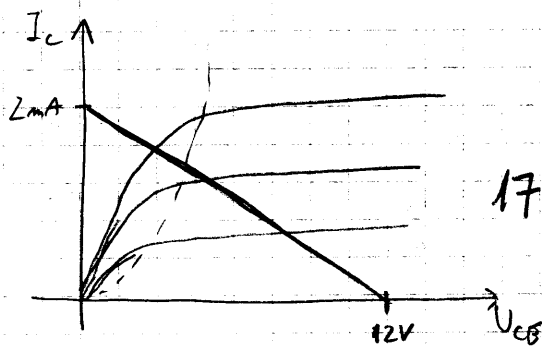- $\beta = 50 \rightarrow I_C = 1 mA, U_{CE} = 6V$
- $\beta = 100 \rightarrow I_C = 0,5 mA, U_{CE} = 9V$
- $\beta = 150 \rightarrow I_C = 1,5 mA, U_{CE} = 3V$




Unipolarni tranzistor

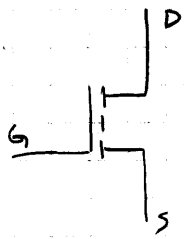

$U_T > 0$

ind. kanal

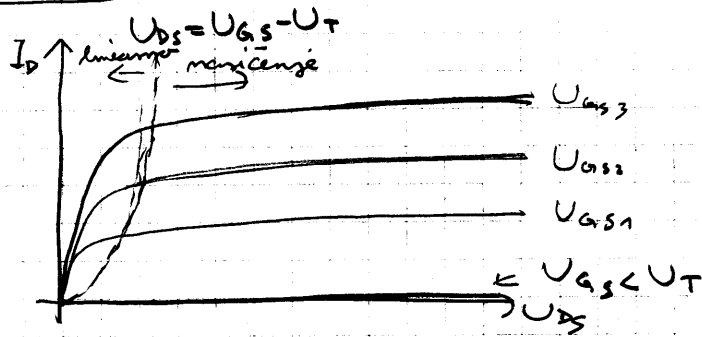


$$I_{Dm} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 (1 + \lambda U_{DS}) \dots \text{nasičenje}$$

Ker konstant. v nasičenju niso
ravnine

$$= \frac{k_n}{2} (U_{GS} - U_T)^2 (1 + \lambda U_{DS}) \quad \therefore k_n = \mu_n C_{ox} \frac{W}{L}$$


$$k_n (U_{GS} - U_T)^2 (1 + \lambda U_{DS}) \quad \dots \quad k_n = \frac{\mu_n C_{ox}}{2} \frac{W}{L}$$
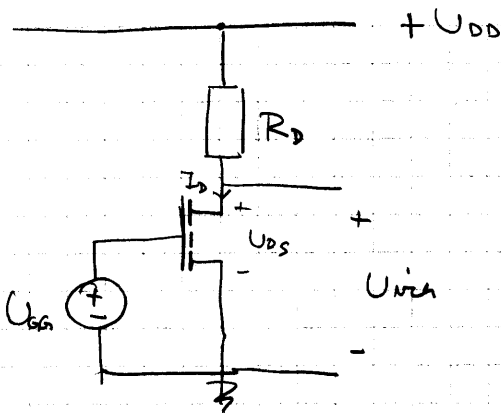
$$I_{Dm} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} [2 \cdot (U_{GS} - U_T) U_{DS} - U_{DS}^2] \dots \text{lin. področje}$$



$$U_{DS} = U_{DD} - I_D R_D$$

$$I_D = \frac{U_{DD} - U_{DS}}{R_D}$$

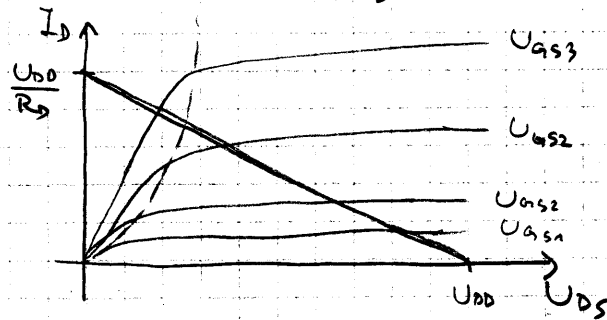


Zapora $U_{GS} < U_T, I_D = 0$

Področje nasičenja $U_{GS} > U_T$
 $U_{DS} > U_{GS} - U_T$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 (1 + \lambda U_{DS})$$

Lin. podr. $U_{GS} > U_T$
 $U_{DS} < U_{GS} - U_T$
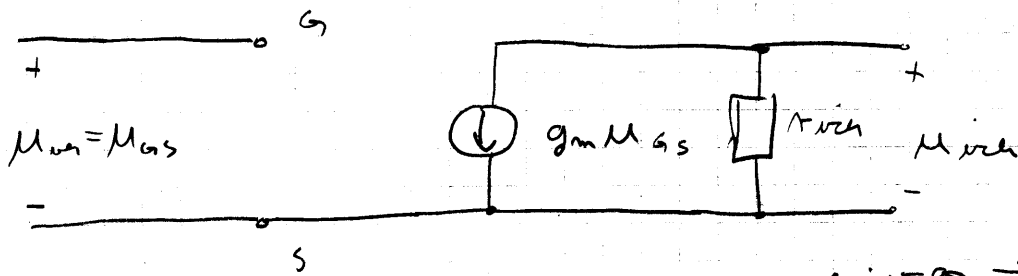
$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} [2(U_{GS} - U_T) U_{DS} - U_{DS}^2]$$



$r_{ohm} = \infty \rightarrow$ kanal. vodljivost ($\lambda = 0$)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 (1 + \lambda U_{DS})$$

$$g_m = \frac{\partial I_D}{\partial U_{GS}} = 2 \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T) \Big|_{U_{GS} = U_{GS}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (U_{GS} - U_T)$$

$$r_{ohm} = \frac{\partial U_{DS}}{\partial I_D}$$


$$\frac{1}{r_{ohm}} = \frac{\partial I_D}{\partial U_{DS}} = \lambda \cdot \underbrace{\frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2}_{\approx I_D}$$

$$r_{ohm} = \frac{1}{\lambda I_D}$$

▣ bracunajte DT in Am za podano vezje

D.T. (I_D, U_{DS})

$$A_m = \frac{U_{ohm}}{U_{gs}}$$

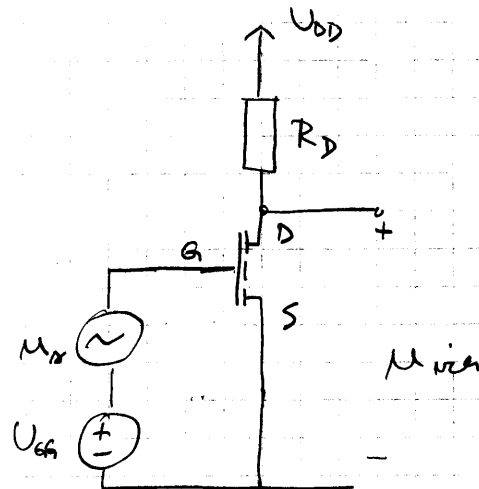

$$U_{DD} = 5V$$

$$R_D = 5k\Omega$$

$$\frac{\mu_n C_{ox}}{2} = 20 \frac{mA}{V^2}$$

$$W = 10 \mu m$$

$$L = 1 \mu m$$

$$U_{GG} = 2V$$

$$U_T = 0,8V$$


$$\lambda = 0$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 = 20 \frac{mA}{V^2} \cdot \frac{10}{1} (2V - 0,8V)^2 = 0,288 mA$$

$$U_{DS} = U_{DD} - I_D R_D = 5V - 0,288 mA \cdot 5k\Omega = 3,56V > 2 - 0,8V \checkmark$$

max. cenj
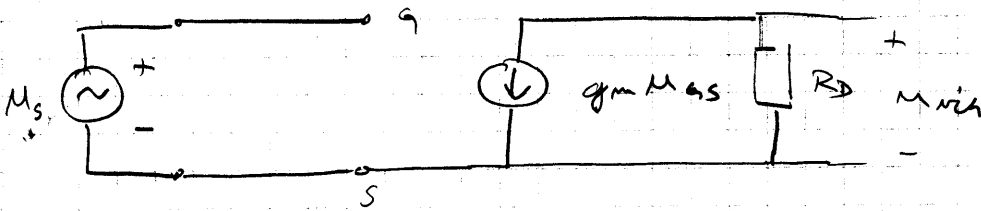
$$g_m = \mu_n C_{ox} \frac{W}{L} (U_{GS} - U_T) = 40 \frac{\mu A}{V^2} \cdot \frac{10}{1} (2V - 0,8V) = 480 \mu S$$



$$u_{vieh} = -g_m u_{gs} R_D$$


$$A_u = -g_m R_D = -480 \frac{\mu A}{V} \cdot 5 k\Omega = -2,4$$

$$U_{GS} = 2V \rightarrow 2,5V:$$

	$U_{GS} = 2V$	$U_{GS} = 2,5V$
I_D	0,288 mA	0,578 mA
U_{DS}	3,65 V	2,1 V
g_m	480 $\mu A/V$	680 $\mu A/V$
A_u	-2,4	-3,4

■ Za podano vežo izračunajte DT, A_u in porabo moči

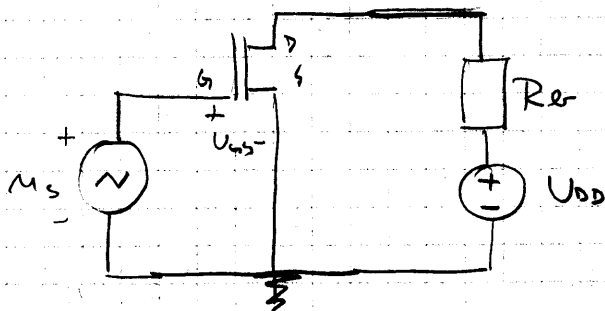D.T. (I_D, U_{DS}), $A_u = \frac{u_{vieh}}{u_s}$, ~~po~~ poraba moči (transistor, breme, baterija)



$$\frac{\mu_n C_{ox}}{2} \frac{W}{L} = 0,2 \frac{mA}{V^2} = k$$

$$U_T = -2V \text{ (negativni kanal)}$$


$$R_D = 20 k\Omega$$

$$u_s = U_{GS} \cos \omega t = 1V \cos \omega t$$

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 = 0,2 \frac{mA}{V^2} \cdot (0V - (-2V))^2 = 0,8 mA$$

20
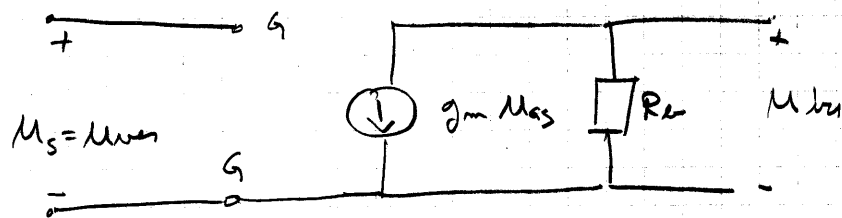
$$U_{DS} = U_{DD} - I_D R_L = 40V - 0,8mA \cdot 20k\Omega = 24V > U_{GS} - U_T$$



$$u_{drain} = -g_m u_{gs} R_L$$

$$A_u = -g_m R_L$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (U_{GS} - U_T) = 0,4 \frac{mA}{V} (0V - (-2V)) = 0,8 \frac{mA}{V}$$

$$A_u = -0,8 \frac{mA}{V} \cdot 20k\Omega = -16$$

Brez nadomestne vezave za majhne signale:

$$u_s = 1V \cdot \cos \omega t$$

$$i_D = k (U_{GS} + u_{gs} - U_T)^2$$

$$= k \left(\underset{0V}{U_{GS}} + 1V \cos \omega t - U_T \right)^2$$

$$= k \cdot (U_{GS} - U_T + 1V \cos \omega t)^2$$

$$= k \left((U_{GS} - U_T)^2 + 2 (U_{GS} - U_T) \cdot 1V \cos \omega t + k \cdot 1V^2 \cos^2 \omega t \right)$$

$$\cos^2 \omega t = \frac{1 + \cos 2\omega t}{2}$$

$$i_D = k (U_{GS} - U_T)^2 + 2k (U_{GS} - U_T) 1V \cos \omega t + k \cdot 1V^2 \frac{1 + \cos 2\omega t}{2}$$

$$= 0,2 \frac{mA}{V^2} \cdot 4V^2 + 2 \cdot 0,2 \frac{mA}{V^2} (2V) \cdot 1V \cos \omega t + 0,2 \frac{mA}{V^2} \cdot \frac{1}{2} \cdot 1V^2 +$$

$$+ 0,2 \frac{mA}{V^2} \cdot \frac{1}{2} \cos 2\omega t \cdot 1V^2$$

$$\approx 0,8mA$$

$$= 0,9mA + 0,8mA \cdot \cos \omega t + 0,1mA \cos 2\omega t$$

$$\begin{aligned}
 u_{DS} &= U_{DD} - R_L \cdot i_D \\
 &= 40V - 20k\Omega (0,9mA + 0,8mA \cos \omega t + 0,1mA \cos 2\omega t) \\
 &= 22V - 16V \cos \omega t - 2V \cos 2\omega t
 \end{aligned}$$

$$A_m = \frac{u_{\max}}{u_{\min}} = \frac{-16V \cos \omega t}{1V \cos \omega t} = \underline{\underline{-16}}$$

~~Popravn~~ Popravnjenje zenadi 2. harmoniske:

$$D_{2,1} = \frac{U_2}{U_1} = \frac{2}{16} = \frac{1}{8} = 12,5\%$$

$$\begin{aligned}
 p_T(t) &= i_D(t) u_{DS}(t) = k \cdot (U_{GS} - U_T + u_{gs})^2 \cdot \underbrace{(U_{DD} - R_L k (U_{GS} - U_T + u_{gs})^2)}_{u_{DS} = U_{DD} - R_L i_D} \\
 &\quad \text{ELN, 16.10.}
 \end{aligned}$$

$$\begin{aligned}
 p_T(t) &= k U_{DD} (U_{GS} - U_T + u_{gs})^2 - k^2 R_L (U_{GS} - U_T + u_{gs})^4 \\
 &= 0,2 \cdot 40 \cdot (2 + \cos \omega t)^2 - 0,2^2 \cdot 20 (2 + \cos \omega t)^4
 \end{aligned}$$

$$\begin{aligned}
 &= 8 \cdot (4 + 4 \cos \omega t + \cos^2 \omega t) - 0,8 (16 + 32 \cos \omega t + \\
 &+ 24 \cos^2 \omega t + 8 \cos^3 \omega t + \cos^4 \omega t)
 \end{aligned}$$

$$= 19,2 + 6,4 \cos \omega t - 11,2 \cos^2 \omega t - 6,4 \cos^3 \omega t - 0,8 \cos^4 \omega t$$

$$\bar{p}_T = \frac{1}{T} \int_0^T p_T(t) dt =$$

$$= \frac{1}{T} \left(19,2 \int_0^T dt + 6,4 \int_0^T \cos \omega t dt - 11,2 \int_0^T \cos^2 \omega t dt - 6,4 \int_0^T \cos^3 \omega t dt - 0,8 \int_0^T \cos^4 \omega t dt \right)$$

$$\int_0^T \cos \omega t dt = 0 \quad \int_0^T \cos^3 \omega t dt = 0 \quad \int_0^T \cos^2 \omega t dt = \frac{T}{2} \quad \int_0^T \cos^4 \omega t dt = \frac{3T}{8}$$

$$\bar{p}_T = \frac{1}{T} \left(19,2T - 11,2 \frac{T}{2} - 0,8 \frac{3T}{8} \right) = 13,3 \text{ mW}$$

$$\text{minoran moc: } P_T = I_D \cdot U_{DS} = 0,8 \text{ mA} \cdot 24 \text{ V} = 19,2 \text{ mW}$$

$$\begin{aligned}
 P_{DD}(t) &= i_D U_{DD} = U_{DD} \cdot k (U_{GS} - U_T + \mu_{gs})^2 \\
 &= 40 \cdot 0,2 (2 + \cos \omega t)^2 \\
 &= 32 + 32 \cos \omega t + 8 \cos^2 \omega t
 \end{aligned}$$

$$\overline{P_{DD}} = \frac{1}{T} \int_0^T P_{DD}(t) dt = \frac{1}{T} (32T + 8 \frac{T}{2}) = 36 \text{ mW}$$

$$P_{DD} = I_D U_{DD} = 0,8 \text{ mA} \cdot 40 \text{ V} = 32 \text{ mW}$$

$$\begin{aligned}
 P_{R_L}(t) &= R_L \cdot i_D^2(t) = R_L k^2 (U_{GS} - U_T + \mu_{gs})^4 \\
 &= 20 \cdot 0,2^2 (2 + \cos \omega t)^4 =
 \end{aligned}$$

$$= 0,8 (16 + 32 \cos \omega t + 24 \cos^2 \omega t + 8 \cos^3 \omega t + \cos^4 \omega t)$$



$$= 12,8 + 25,6 \cos \omega t + 19,2 \cos^2 \omega t + 6,4 \cos^3 \omega t + 0,8 \cos^4 \omega t$$

$$\overline{P_{R_L}} = \frac{1}{T} \int_0^T P_{R_L}(t) dt = 22,7 \text{ mW}$$

$$P_{R_L} = R_L \cdot I_D^2 = 20 \cdot 0,8^2 = 12,8 \text{ mW}$$

MOČ	MIROVNA		DELOVNA	
	mW	%	mW	%
TRANZISTOR	19,2	60	13,3	37
UPOR	12,8	40	22,7	63
BATERIJA	32	100	36	100

■ Iračunajte DT. (I_D, U_{GS}), $A_v = \frac{u_{i\text{ch}}}{u_s}$ in maks. amplitudo $|U_s|_{\text{max}}$ (preč $u + \rightarrow$ lin. podr., preč $u - \rightarrow$ rapora)

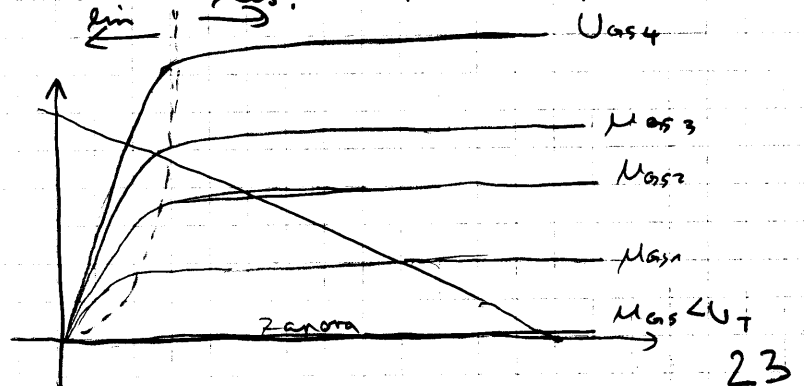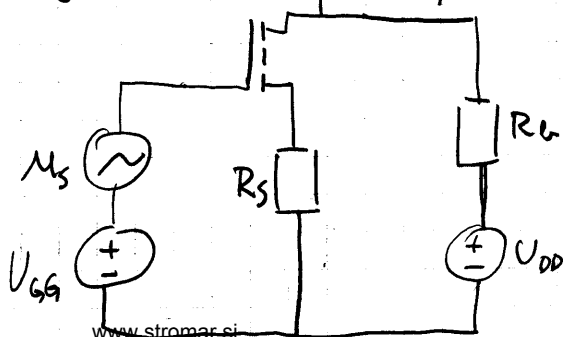

$$U_T = 2V$$

$$U_{GG} = 5V$$

$$R_S = 1k\Omega$$

$$R_L = 15k\Omega$$

$$k = \frac{\mu_m C_{ox}}{2} \frac{W}{L} = 0.25 \frac{mA}{V^2}$$

$$U_{DD} = 30V$$

D.T., A_u , $|U_s|_{max}$

$$I_D = k(U_{GS} - U_T)^2$$

$$U_{GS} = U_{GG} - U_{RS} = U_{GG} - I_D R_S$$

$$U_{GS} = U_{GG} - R_S k (U_{GS} - U_T)^2$$

$$U_{GS} = U_{GG} - R_S k (U_{GS}^2 - 2U_{GS}U_T + U_T^2)$$

$$U_{GS} = U_{GG} - R_S k U_{GS}^2 + 2R_S k U_{GS}U_T - R_S k U_T^2$$

$$R_S k U_{GS}^2 + U_{GS}(1 - 2R_S k U_T) + R_S k U_T^2 - U_{GG} = 0$$

$$U_{GS1,2} = \frac{-(1 - 2R_S k U_T) \pm \sqrt{(1 - 2R_S k U_T)^2 - 4R_S k (R_S k U_T^2 - U_{GG})}}{2R_S k}$$

$$= \underline{\underline{4V}} \quad (\text{mit } -4V \text{ is reponi})$$


$$U_{GS} = 4V$$

$$I_D = k(U_{GS} - U_T)^2 = 0.25(4 - 2)^2 = \underline{\underline{1mA}}$$

$$U_{DS} = U_{DD} - R_L I_D - R_S I_D = \underline{\underline{14V}}$$

$$14V > 4V - 2V = 2V \quad \checkmark \quad \text{marginje}$$

$$g_m = 2k(U_{GS} - U_T) \Big|_{U_{GS}=U_{GS}} = 2 \cdot 0.25 \frac{mA}{V^2} (4V - 2V) = 1mS$$

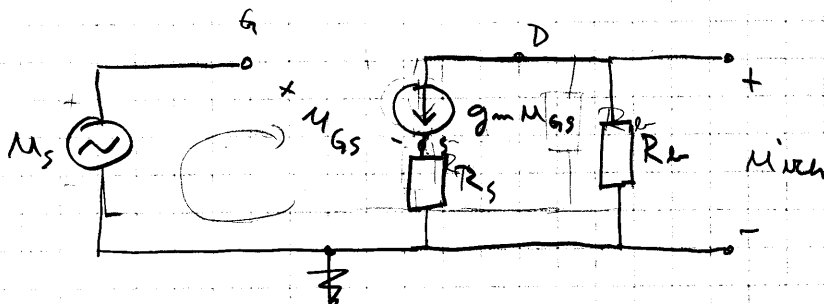


$$A_u = \frac{U_{misch}}{U_s}$$

$$U_{misch} = -R_{eq} g_m U_{GS}$$

$$U_{GS} + U_{RS} = U_s \Rightarrow U_{GS} + g_m U_{GS} R_S = U_s \Rightarrow U_{GS} = \frac{U_s}{1 + g_m R_S}$$

$$U_{misch} = \frac{R_{eq} g_m}{1 + g_m R_S} U_s$$
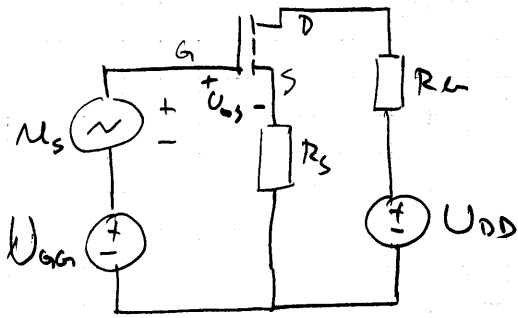
$$A_m = -\frac{R_L \cdot g_m}{1 + R_S g_m} = \underline{\underline{-7,5}}$$



$$U_{GG} = 5V$$


$$U_T = 2V$$

Ko se tranzistor razne:

$$U_{GS} = U_T, I_D = 0 \Rightarrow U_{RS} = 0$$

$$U_{GS} = U_{GG} + U_S$$

$$2V = 5V + U_S \Rightarrow U_S = -3V$$

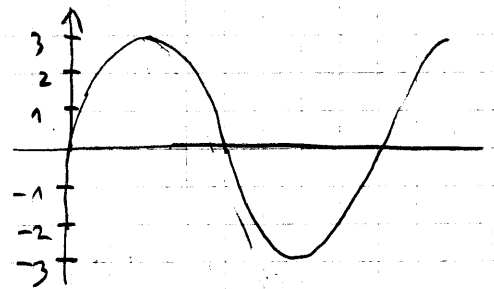

$$|U_{Smax}| = 3V$$

Ko opre tranz. v linearni območje

$$U_{DS} = U_{GS} - U_T$$

$$U_{DS} = U_{DD} - I_D(R_L + R_S) = U_{GS} - U_T$$

$$U_{DD} - I_D(R_L + R_S)(U_{GS} - U_T) = U_{GS} - U_T$$

$$30 - 0,25 \cdot (U_{GS} - 2)^2 (15 + 1) = U_{GS} - 2$$

$$32 - (0,25U_{GS}^2 - U_{GS} + 1) \cdot 16 = U_{GS}$$

$$-4U_{GS}^2 + 15U_{GS} + 16 = 0$$

$$U_{GS1,2} = \frac{-15 \pm \sqrt{15^2 + 4 \cdot 4 \cdot 16}}{-8} = \begin{cases} -0,866V // \text{ker } U_{GS} > U_T \\ +4,616V \checkmark \end{cases}$$

$$U_{GS} = 4,616V$$

$$I_D = \frac{\mu_m C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 = 1,711 \text{ mA}$$

$$U_{RS} = I_D \cdot R_S = 1,711 \text{ mA} \cdot 1k\Omega = 1,711V$$

$$-U_{GS} - \mu_s + U_{GS} + U_{RS} = 0$$


$$\overline{\mu_s} = U_{RS} + U_{GS} - U_{GS} = 1,327V$$

$$\underline{\mu_s} = -3V$$

$$|\mu_s|_{MAX} = 1,327V$$

ELN, 23.11.

☑ Za podano vezje nrt. D.T., Am in $|\mu_s|_{MAX}$

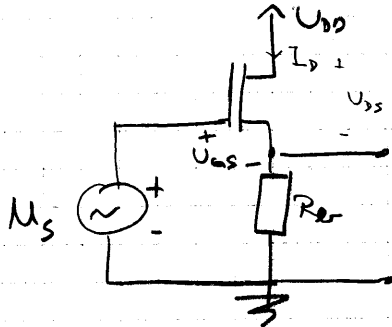

$$U_{DD} = 5V$$

$$\frac{\mu_m C_{ox}}{2} \frac{W}{L} = 0,5 \frac{mA}{V^2}$$

$$U_T = -1V$$

$$R_s = 10k\Omega$$

$$I_D = \frac{\mu_m C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2$$

$$-U_{GS} = U_{RS} = I_D \cdot R_s$$

$$U_{GS} = -0,5 \frac{mA}{V^2} (U_{GS} - (-1V))^2 \cdot 10k\Omega$$

$$U_{GS} = -5 \frac{A}{V^2} (U_{GS} + 1V)^2 \frac{V}{A}$$

$$U_{GS} = -5 (U_{GS}^2 + 2U_{GS} + 1)$$

$$5U_{GS}^2 + 11U_{GS} + 5 = 0$$


$$U_{GS1,2} = \frac{-11 \pm \sqrt{121 - 4 \cdot 5 \cdot 5}}{2 \cdot 5} = \begin{cases} -0,6417V \checkmark \\ -1,5858V \checkmark \end{cases}$$

$$U_{GS} = -0,6417V$$

$$I_D = \frac{\mu_m C_{ox}}{2} \frac{W}{L} (U_{GS} - U_T)^2 = 64,17 \mu A$$

$$U_{DS} = U_{DD} - I_D R_L = U_{DD} - U_{RS} = U_{DD} + U_{GS} = 4,358V$$

$$4,358V \checkmark - 0,6417V - (-1V) \checkmark$$

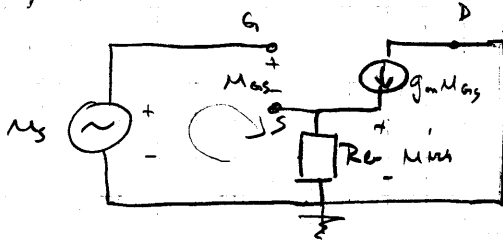A_u:

$$A_u = \frac{u_{\text{ich}}}{u_s}$$

$$u_{\text{ich}} = u_{R_L} = g_m u_{GS} R_L$$

$$-u_s + u_{GS} + u_{R_S} = 0$$

$$-u_s + u_{GS} + g_m u_{GS} R_L = 0$$

$$u_{GS} = \frac{u_s}{1 + g_m R_L}$$

$$u_{\text{ich}} = \frac{g_m R_L}{1 + g_m R_L} u_s$$

$$A_u = \frac{g_m R_L}{1 + g_m R_L}$$

$$g_m = 2 \frac{\mu_m C_{ox}}{2} \frac{W}{L} (u_{GS} - U_T) \Big|_{u_{GS} = u_s} = 1 \frac{\text{mA}}{\text{V}^2} (-0,6 + 1,7 \text{V} + 1 \text{V})$$

$$= 0,358 \text{ mS}$$

$$A_u = 0,48$$

 $|u_s|_{\text{max}}$:Transistor ne razpne: $u_{GS} \leq U_T$

$$I_D = 0 \rightarrow u_{GS} = u_s$$

$$u_s = u_T = -1 \text{V} = \underline{u_s}$$

Lim področje: $u_{DS} = u_{GS} - U_T$

$$u_{DS} = u_{DD} - u_{R_L} = u_{DD} - k (u_{GS} - U_T)^2 R_L$$

$$u_{DD} - k (u_{GS} - U_T)^2 R_L = u_{GS} - U_T$$

$$U_{GS} - U_T = X$$

$$U_{DS} \rightarrow R_E \quad 10 \text{ k}\Omega \quad 0,5 \frac{\text{mA}}{\sqrt{2}} X^2 + X - 5 \text{V} = 0$$

$$5X^2 + X - 5 = 0$$

$$X_{1,2} = \frac{-1 \pm \sqrt{1 + 4 \cdot 5 \cdot 5}}{2 \cdot 5} = \begin{cases} 0,905 \text{V} \checkmark & U_{GS} > U_T \rightarrow X > 0 \\ -1,1 \text{V} // & \end{cases}$$

$$U_{GS} - U_T = 0,905 \text{V}$$

$$U_{GS} = -0,095 \text{V}$$


$$U_{RE} = R_E \cdot I_D = R_E \frac{I_{D, \text{max}}}{2} \frac{W}{L} (U_{GS} - U_T)^2 = 4,095 \text{V}$$

$$U_S = U_{GS} + U_{RE} = 4 \text{V} = \sqrt{u_s}$$

$$I_{S, \text{max}} = 1 \text{V}$$

Dvostopenjske vezave

Emitorsko sklopljen par

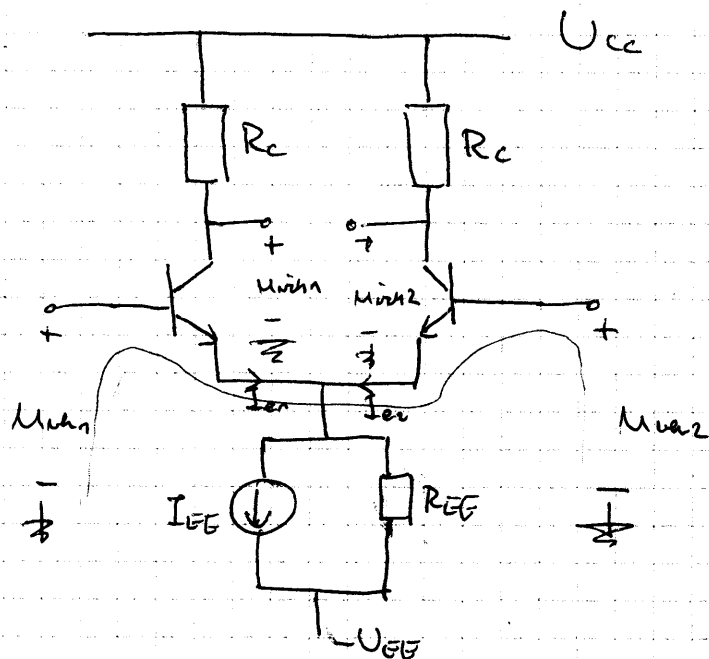

$$U_{BE1} - U_{BE1} + U_{BE2} - U_{BE2} = 0$$

$$U_{BE1} - U_{BE2} = U_{BE1} - U_{BE2}$$

$$I_C = I_S e^{\frac{U_{BE}}{U_T}}$$

$$\frac{I_C}{I_S} = e^{\frac{U_{BE}}{U_T}}$$

$$\ln \frac{I_C}{I_S} = \frac{U_{BE}}{U_T}$$

$$U_{BE} = U_T \ln \frac{I_C}{I_S}$$

$$U_{BE1} = U_T \ln \frac{I_{C1}}{I_{S1}}$$

$$U_{BE2} = U_T \ln \frac{I_{C2}}{I_{S2}}$$

Pr $I_{s1} = I_{s2}$

$$\frac{I_{c1}}{I_{c2}} = e^{\frac{U_{BE1} - U_{BE2}}{U_T}} = e^{\frac{U_{vch1} - U_{vch2}}{U_T}} = \frac{I_{c1}}{I_{c2}}$$


Zamenajmo tuk sicer R_{EE}

$$I_{c1} + I_{c2} = I_{EE} = \frac{1}{\alpha} (I_{c1} + I_{c2})$$

$$I_{c1} = \frac{\alpha \cdot I_{EE}}{1 + e^{-\frac{U_{vch\ diff}}{U_T}}}$$

$$U_{vch1} - U_{vch2} = U_{vch\ diff}$$
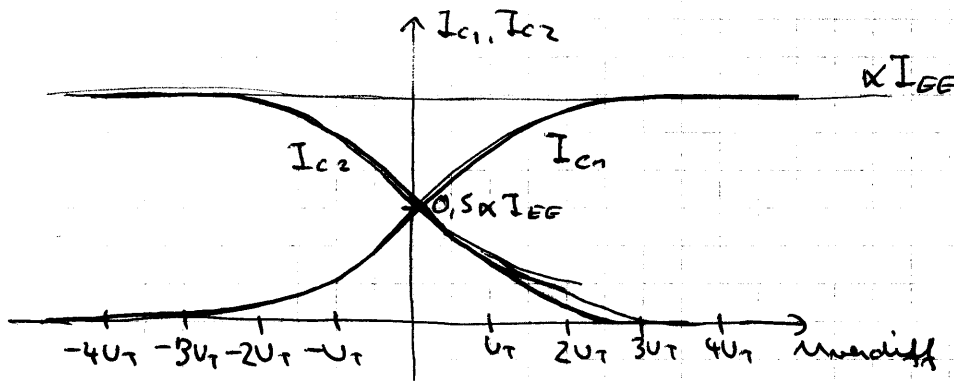
$$I_{c2} = \frac{\alpha I_{EE}}{1 + e^{\frac{U_{vch\ diff}}{U_T}}}$$




$$U_{vch1} = U_{cc} - I_{c1} R_c$$


$$U_{vch2} = U_{cc} - I_{c2} R_c$$

$$U_{vch\ diff} = U_{vch1} - U_{vch2} = \alpha I_{EE} R_c \tanh\left(-\frac{U_{vch\ diff}}{2U_T}\right)$$
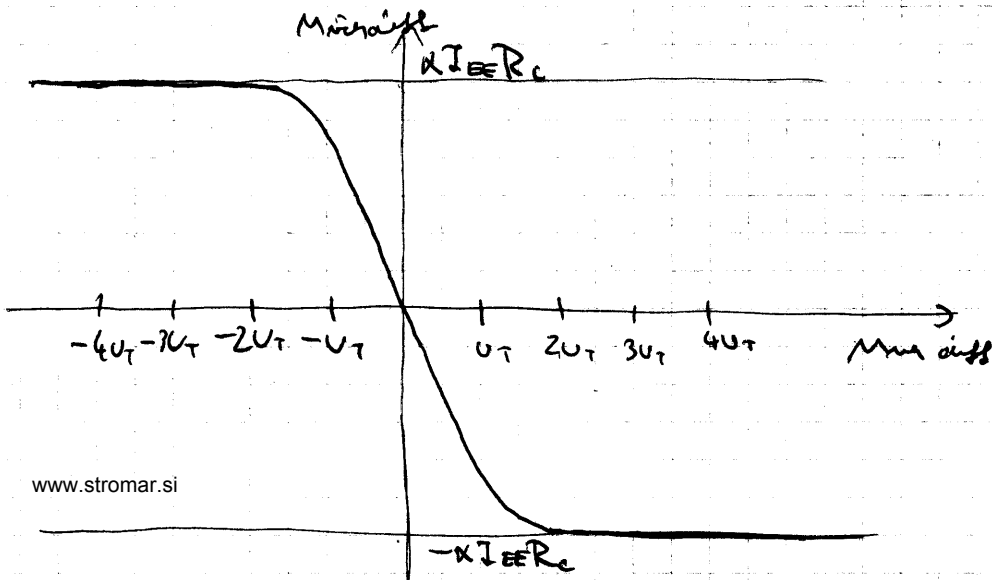
$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} = \frac{e^{2x} - 1}{e^{2x} + 1} = \frac{2}{e^{-2x} + 1} - 1$$



malenični model:

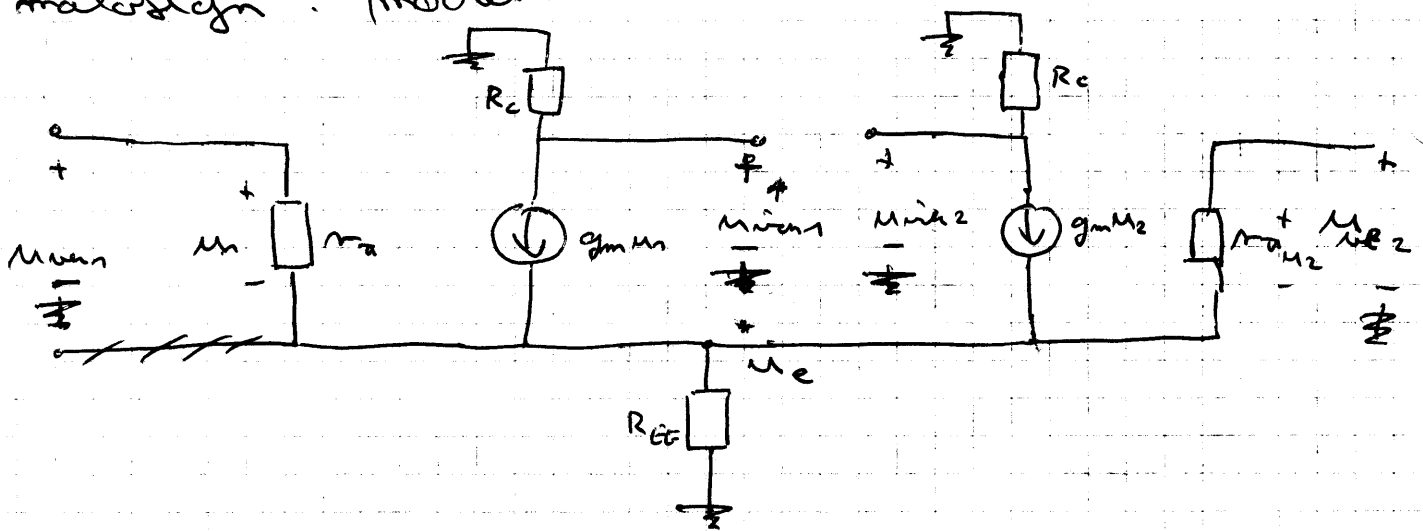

$$\frac{u_{in1} - u_e}{r_{\pi}} + g_m(u_{in1} - u_e) + g_m(u_{in2} - u_e) + \frac{u_{in2} - u_e}{R_{L2} r_{\pi}} = \frac{u_e}{R_{EE}}$$

$$u_e = \frac{u_{in1} + u_{in2}}{2 + \frac{1}{g_m R_{EE} (1 + \frac{1}{\beta})}}$$

$$u_{i\check{c}h1} = -g_m u_{in1} R_c = -g_m R_c (u_{in1} - u_e)$$

$$u_{i\check{c}h2} = -g_m u_{in2} R_c = -g_m R_c (u_{in2} - u_e)$$

∴ preprostimo matematikam

inženirski način:

$$u_{i\check{c}h dif} = u_{i\check{c}h1} - u_{i\check{c}h2}$$

$$u_{i\check{c}h skup} = \frac{u_{i\check{c}h1} + u_{i\check{c}h2}}{2}$$

$$u_{i\check{c}h1} = \frac{u_{i\check{c}h dif}}{2} + u_{i\check{c}h skup}$$

$$u_{i\check{c}h2} = -\frac{u_{i\check{c}h dif}}{2} + u_{i\check{c}h skup}$$



$$u_{i\check{c}h dif} = u_{i\check{c}h1} - u_{i\check{c}h2}$$

$$u_{i\check{c}h skup} = \frac{u_{i\check{c}h1} + u_{i\check{c}h2}}{2}$$

$$\Rightarrow \begin{aligned} u_{i\check{c}h1} &= \frac{u_{i\check{c}h dif}}{2} + u_{i\check{c}h skup} \\ u_{i\check{c}h2} &= -\frac{u_{i\check{c}h dif}}{2} + u_{i\check{c}h skup} \end{aligned}$$

Protiformo kermiljenje:

ELN, 9.11.

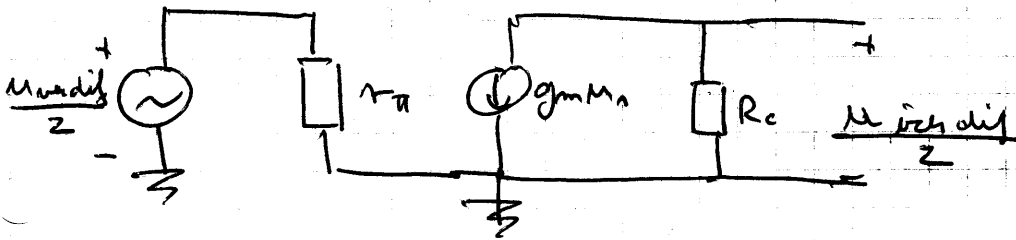
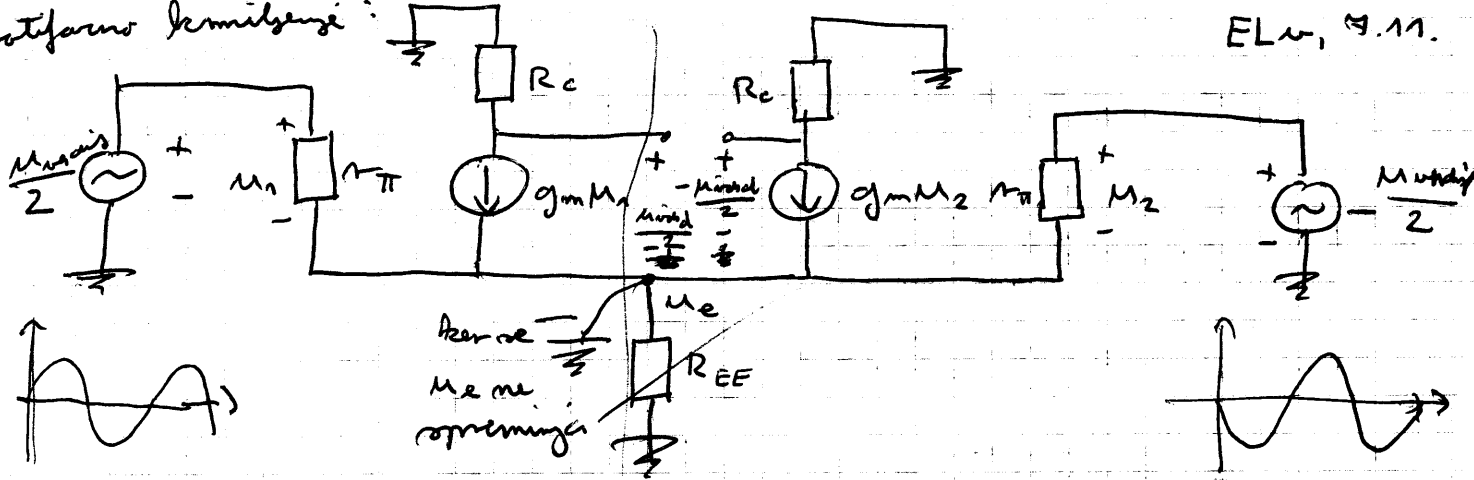


$$\frac{u_{\text{ich,dif}}}{2} = -g_m u_{\text{in}} R_c = -g_m R_c \frac{u_{\text{in,dif}}}{2}$$

$$A_{dm} = -g_m R_c = \frac{u_{\text{ich,dif}}}{u_{\text{in,dif}}}$$

differential mode

Sufornno kermiljenje:

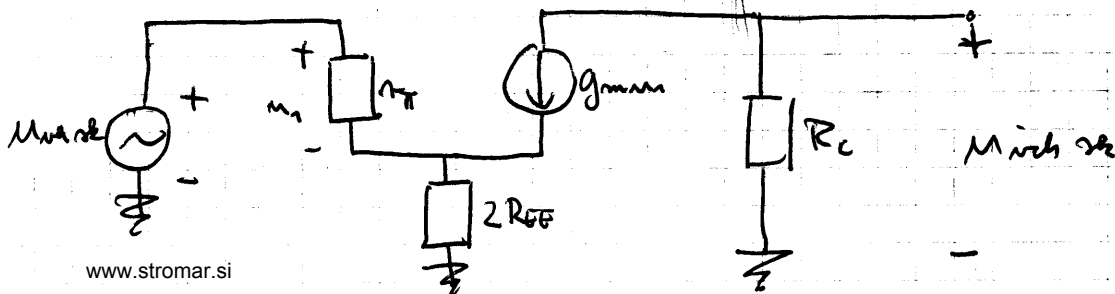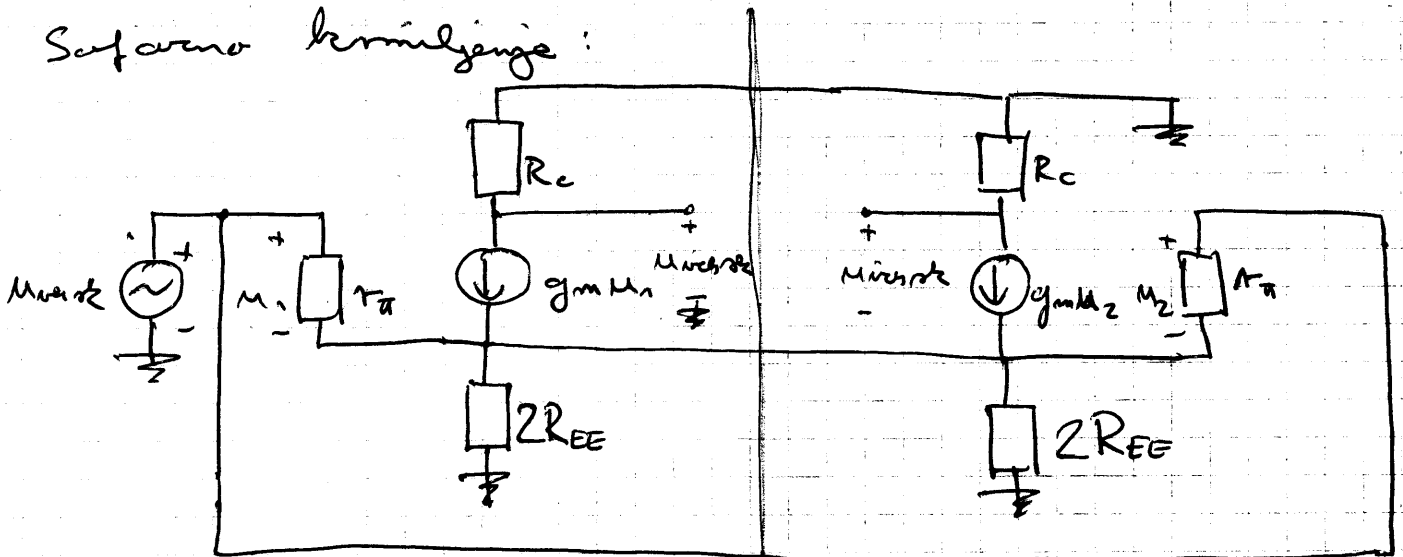

$$M_{u_{n2}} - \beta i_b R_c - (\beta + 1) 2 R_{EE} = 0$$

$$i_b = \frac{M_{u_{n2}}}{r_{\pi} + 2 R_{EE} (\beta + 1)}$$

$$u_{n2} = -\beta i_b R_c = -\frac{\beta R_c}{r_{\pi} + 2 R_{EE} (\beta + 1)} M_{u_{n2}}$$

common mode

$$A_{cm} = \frac{M_{u_{n2}}}{M_{u_{n1}}} = -\frac{\beta R_c}{r_{\pi} + 2 R_{EE} (\beta + 1)} = -\frac{g_m R_c}{1 + 2 g_m R_{EE} (1 + \frac{1}{\beta})}$$

$g_m = \frac{\beta}{r_{\pi}}$

$$A_{cm} = -\frac{g_m R_c}{1 + 2 g_m R_{EE} (1 + \frac{1}{\beta})}$$

COMMON MODE REJECTION RATIO


$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{g_m R_c}{g_m R_c} \cdot \frac{1 + 2 g_m R_{EE} (1 + \frac{1}{\beta})}{1} = 1 + 2 g_m R_{EE} (1 + \frac{1}{\beta})$$

- rejection factor


$$CMRR = 1 + 2 g_m R_{EE} (1 + \frac{1}{\beta})$$

$$M_{u_{n1}} = \frac{M_{u_{in1}}}{2} + M_{u_{n2}}$$
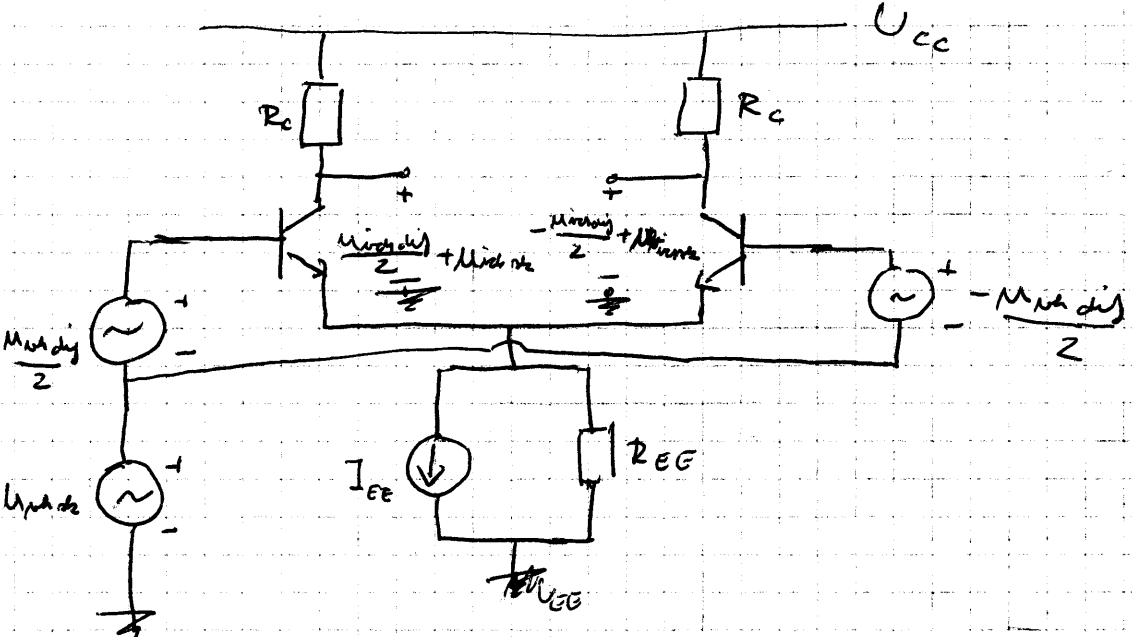
$$M_{u_{n2}} = -\frac{M_{u_{in1}}}{2} + M_{u_{n2}}$$



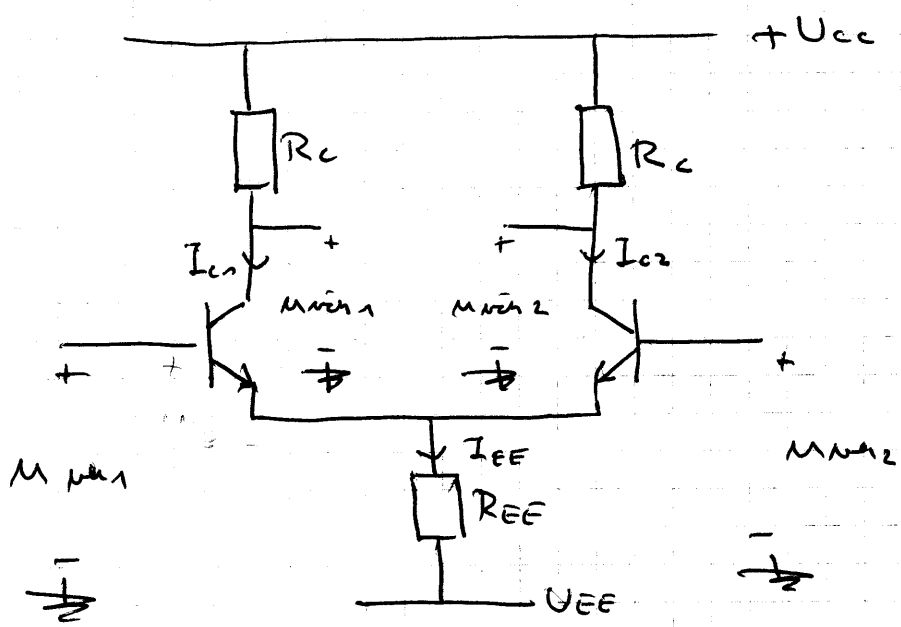Za podana vezje izračunajte rejekcijski faktor



$U_{CC} = 15V$
 $U_{EE} = -15V$
 $R_C = R_{EE} = 10k\Omega$
 $\beta \rightarrow \infty (I_B \rightarrow 0)$
 $U_{BE} = 0,7V$

$$CMRR = 1 + 2g_m R_{EE}$$

$$g_m = \frac{I_C}{U_T}$$

$$I_{EE} = I_{C1} + I_{C2} = 2I_C \Rightarrow I_C = \frac{I_{EE}}{2}$$


$$I_{EE} = \frac{U_E - U_{EE}}{R_{EE}} = \frac{-U_{BE} - U_{CE}}{R_{EE}} = 1,43 \text{ mA}$$

$$CMRR = 1 + 2 \frac{I_C}{U_T} R_{EE} = 1 + 2 \frac{I_{EE}}{2} \frac{1}{U_T} R_{EE} = 1 + I_{EE} \cdot \frac{1}{U_T} R_{EE} = 551$$

$$CMRR_{dB} = 20 \log CMRR = 54,8 \text{ dB}$$

$$\bar{I}_c \approx \text{konstanta} \Rightarrow I_C = I_C \frac{1+\beta}{\beta} = \frac{I_C}{\alpha}$$

(7)

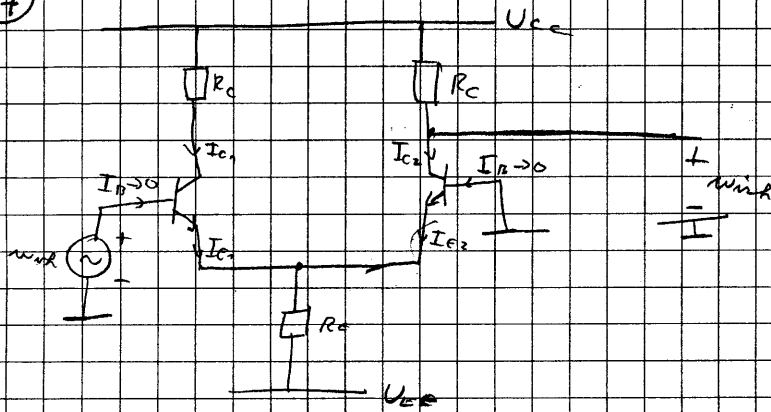

$$U_{CC} = 15V$$

$$U_{EE} = -15V$$

$$R_C = 10 \text{ k}\Omega$$

$$R_E = 15,3 \text{ k}\Omega$$

$$U_{BE} = 0,7V$$

$$\beta \rightarrow \infty$$

$$A_u = \frac{u_{wirk}}{u_{wird}}$$

$$I_{E1} + I_{E2} = I_{RE} = \frac{U_{BE}}{R_E} = \frac{-U_{BE} - U_{EE}}{R_E} = \frac{-0,7V - (-15)V}{15,3 \text{ k}\Omega} = 1 \text{ mA}$$

$$I_{E1} = I_{E2} = 0,5 \text{ mA} = I_{C1} = I_{C2} = I_C$$

$$A_{dm} = -g_m R_C = -\frac{I_C}{U_T} \cdot R_C = -\frac{0,5 \text{ mA}}{26 \text{ mV}} \cdot 10 \text{ k}\Omega = -192,3$$

$$A_{cm} = -\frac{g_m R_C}{1 + 2g_m R_E (1 + \frac{1}{\beta})} = -\frac{g_m R_C}{1 + 2g_m R_E} = -0,35$$

$$u_{wird} = u_{wird1} = -\frac{u_{wird1}}{2} + u_{wird2}$$

$$u_{wird} = -\frac{1}{2} A_{dm} u_{wird} + A_{cm} u_{wird}$$

$$u_{wird} = -\frac{1}{2} A_{dm} u_{wird} + A_{cm} u_{wird}$$

$$u_{wird1} = u_{wird2} - u_{wird2} = u_{wird}$$


$$u_{wird} = \frac{u_{wird}}{2}$$

$$A_u = \frac{u_{wird}}{u_{wird}} = -\frac{1}{2} A_{dm} + \frac{1}{2} A_{cm} = 95,98$$


35

(str. 34 ne obstaja)

8) Sklopljeni par JFET tranzistorjev

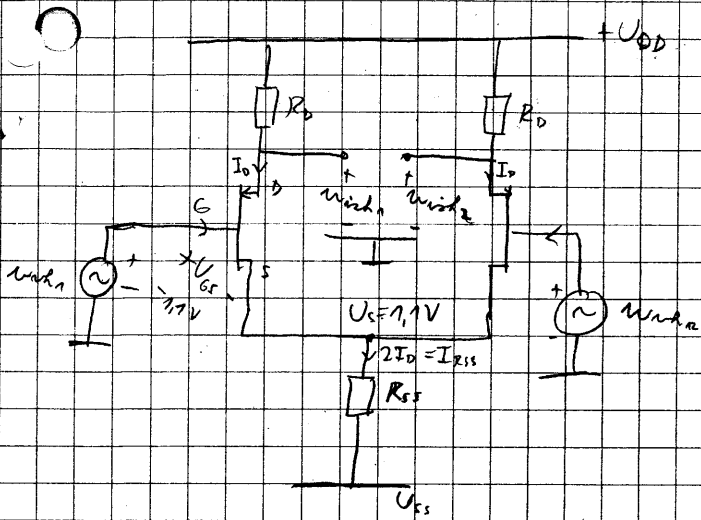

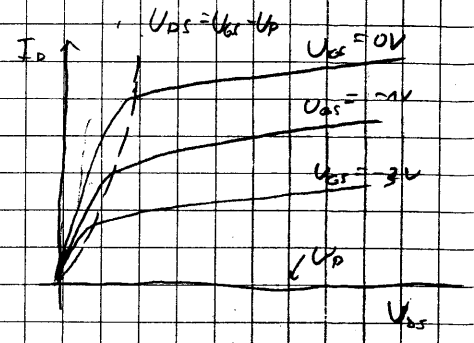- $U_{DD} = 15V$
- $U_{SS} = -15V$
- $R_D = 10k\Omega$
- $R_{SS} = 20k\Omega$
- $U_P = -2V$
- $I_{DSS} = 2mA$
- $CMRR = 2$



$$I_D = I_{DSS} \left(1 - \frac{U_{GS}}{U_P}\right)^2$$

$$g_m = \frac{\partial I_D}{\partial U_{GS}} = -2 I_{DSS} \left(\frac{1}{U_P}\right) \cdot \left(1 - \frac{U_{GS}}{U_P}\right) \Big|_{U_{GS} = U_{GS,OT}} = -\frac{2 I_{DSS} \left(1 - \frac{U_{GS}}{U_P}\right)}{U_P} \Big|_{D.T.}$$

Pracunajino D.T.:

$$0 = U_{GS} + U_{R_{SS}} + U_{SS}$$

$$-U_{GS} = 2 I_D R_{SS} + U_{SS}$$

$$I_D = I_{DSS} \left(1 - \frac{U_{GS}}{U_P}\right)^2$$

$$\sqrt{\frac{I_D}{I_{DSS}}} = 1 - \frac{U_{GS}}{U_P} \Rightarrow U_{GS} = U_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$-U_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) = 2 I_D R_{SS} + U_{SS}$$

$$1 - \sqrt{\frac{I_D}{I_{DSS}}} = \frac{2 I_D R_{SS} + U_{SS}}{U_P}$$

$$1 + \frac{2 I_D R_{SS} + U_{SS}}{U_P} = \sqrt{\frac{I_D}{I_{DSS}}}$$

$$1 + \frac{2(2 I_D R_{SS} + U_{SS})}{U_P} + \left(\frac{2 I_D R_{SS} + U_{SS}}{U_P}\right)^2 = \frac{I_D}{I_{DSS}}$$

Pracunajino enačbo $\Rightarrow I_D = 0,805mA$
(neg. net. proud. negativno odpre)

$$U_{GS} = U_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$U_{GS} = -2V \left(1 - \sqrt{\frac{0,805mA}{2mA}}\right) = -1,1V$$

$$I_{R_{SS}} = \frac{U_{GS} - U_{SS}}{R_{SS}} = \frac{1,1V - (-15V)}{20k\Omega} = 0,805mA$$

$$g_m = \frac{2 I_{DSS} \left(1 - \frac{U_{GS}}{U_P}\right)}{U_P} \Big|_{U_{GS} = -1,1V} = 0,89mS$$


$$A_{dm} = g_m R_D = -8,9$$

$$A_{cm} = -\frac{g_m R_D}{1 + g_m R_{SS} \left(1 + \frac{R_D}{R_{SS}}\right)} \Big|_{R_{in} I_D = 0} = -0,25$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \frac{8,9}{0,25} = 37$$

$$CMRR_{dB} = 31,38dB$$

9)

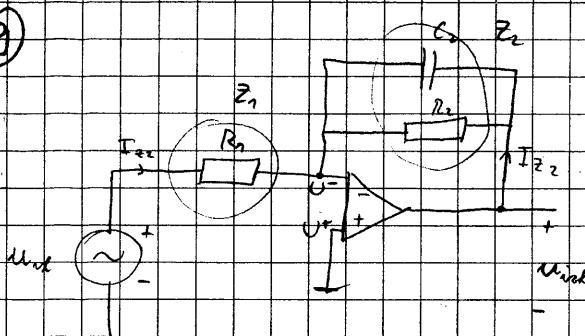

$$I_{z1} = \frac{u_{in} - U^-}{Z_1} = \frac{u_{in}}{Z_1}$$

$$I_{z2} = \frac{u_{out} - U^-}{Z_2} = \frac{u_{out}}{Z_2}$$

$$I_{z1} = -I_{z2} \Rightarrow \frac{u_{in}}{Z_1} = -\frac{u_{out}}{Z_2}$$

$A_u = -\frac{Z_2}{Z_1}$ (za njeležino in predpostavit: $A \rightarrow \infty \Rightarrow u_{in}^- = u_{out}^+ \rightarrow 0$)


$$Z_2 = \frac{1}{Y_2} = \frac{1}{\left(\frac{1}{R_2} + j\omega C_2\right)} = \frac{1}{\frac{1 + j\omega R_2 C_2}{R_2}}$$

$I_{in}^- = I_{in}^+ = 0$ $u_{in}^- = u_{in}^+$
 $u_{in} = A(u_{in}^+ - u_{in}^-)$
 $\downarrow \infty \downarrow 0$

$$A_u = -\frac{Z_2}{Z_1} = \frac{R_2}{(1 + j\omega R_2 C_2) R_1} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C_2}$$

Bodejev diagram:
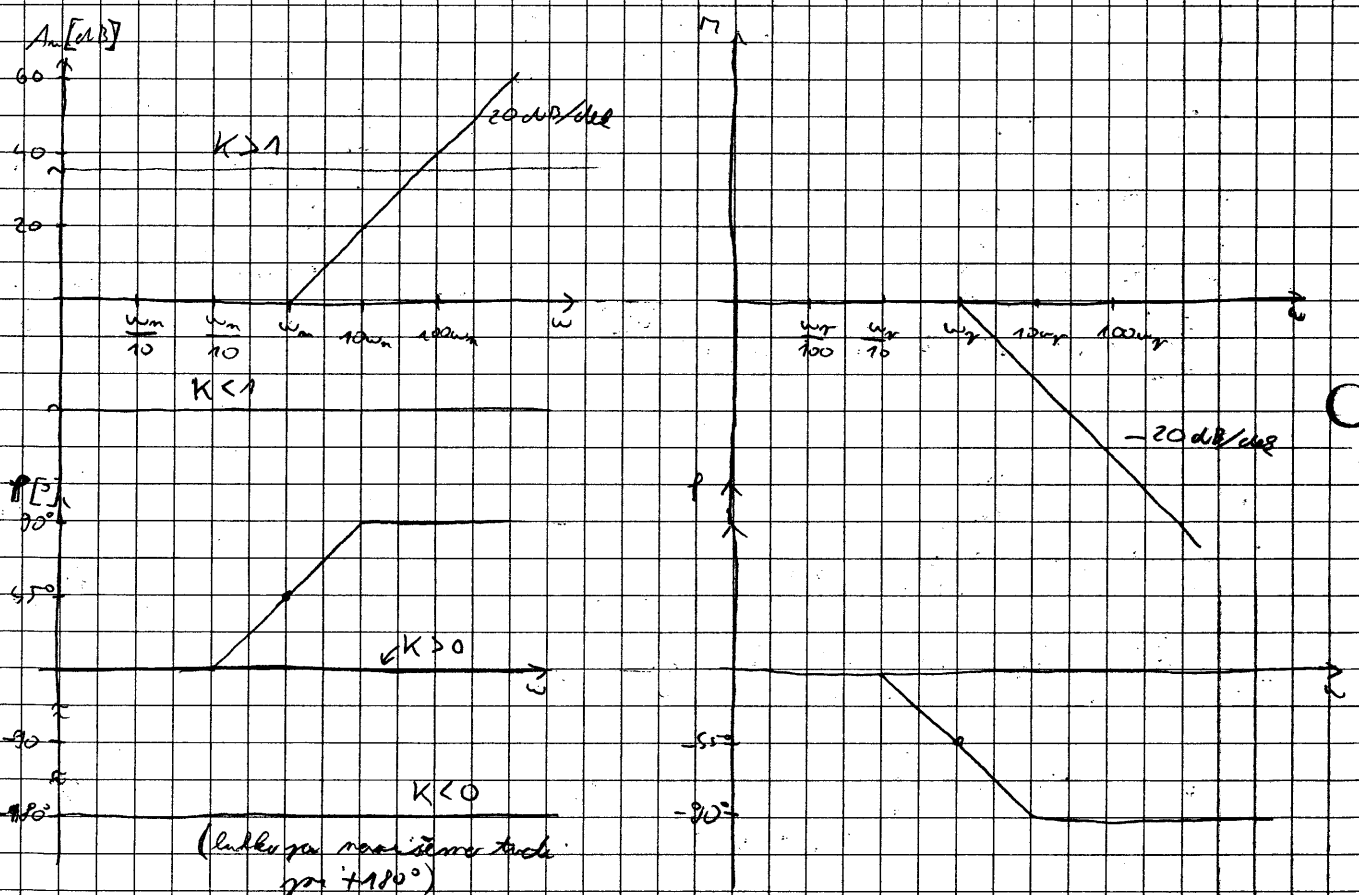
$$A(j\omega) = K \frac{(1 + \frac{j\omega}{\omega_{p1}})(1 + \frac{j\omega}{\omega_{p2}}) \dots (1 + \frac{j\omega}{\omega_{zn1}})}{(1 + \frac{j\omega}{\omega_{z1}})(1 + \frac{j\omega}{\omega_{z2}}) \dots (1 + \frac{j\omega}{\omega_{p3}})}$$



$\tilde{u} \left(1 + \frac{j\omega}{\omega}\right)^n \Rightarrow n$ stopnja

Kako dolžna zbirna oblika na rezonance BD?

ELN 17.12.


Primer:

$$A_m = \frac{1 + R_2 + j\omega C_2}{R + \frac{1}{j\omega C_1}} = \frac{(1 + R_2) \left(1 + \frac{j\omega C_2}{1 + R_2}\right) \cdot j\omega C_1}{j\omega R C_1 + 1} =$$

$$= \frac{(1 + R_2) j\omega C_1 \left(1 + \frac{j\omega R_2 C_2}{1 + R_2}\right)}{1 + \frac{j\omega}{R C_1}} = \frac{C(1 + R_2) \left(1 + \frac{j\omega R_2 C_2}{1 + R_2}\right)}{\left(1 + \frac{j\omega}{R C_1}\right)}$$

- nallon 20dB/dec, - nala x 0,5 gr 10⁵, - faza 90°

(10)

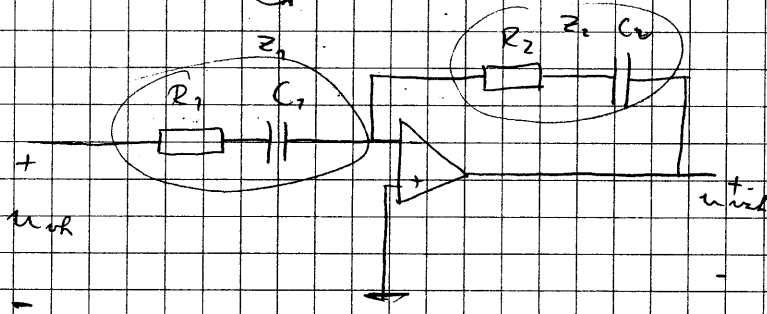

- $R_1 = 1 \text{ k}\Omega$
- $R_2 = 10 \text{ k}\Omega$
- $C_1 = 1 \text{ nF}$
- $C_2 = 100 \text{ nF}$

$$A_m = \frac{Z_2}{Z_1} = \frac{R_2 + \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = \frac{j\omega C_2 R_2 + 1}{j\omega C_1 R_1 + 1}$$

$$Z_2 = R_2 + \frac{1}{j\omega C_2}$$


$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$= \frac{1 + j\omega R_2 C_2}{1 + j\omega R_1 C_1} \cdot \frac{j\omega C_1}{j\omega C_1} = \frac{C_1 \left(1 + \frac{j\omega R_2 C_2}{R_1 C_1}\right)}{1 + \frac{j\omega}{R_1 C_1}}$$

$$\frac{C_1}{C_2} = \frac{1 \text{ nF}}{100 \text{ nF}} = 0,01 = 10^{-2} \cdot \frac{1 + \frac{j\omega}{10^3}}{1 + \frac{j\omega}{10^5}}$$


$$\omega_{ns} = \frac{1}{R_2 C_2} = \frac{1}{10^{-2} \cdot 10 \cdot 10^{-8}} = 10^3$$
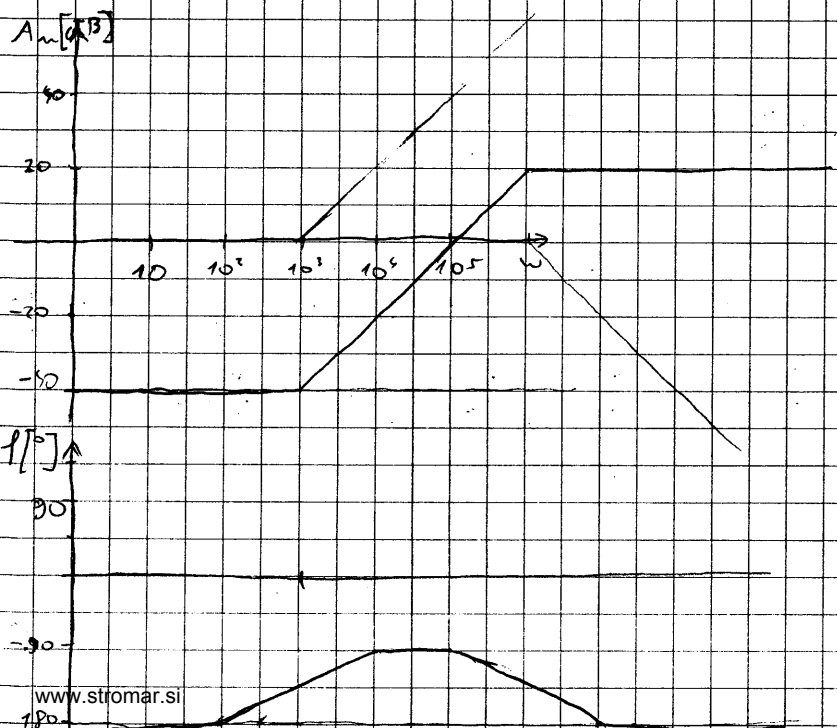
$$\omega_{ps} = \frac{1}{R_1 C_1} = \frac{1}{10 \cdot 1 \cdot 10^{-9}} = 10^6$$



$$A_{mid} = \frac{R_2}{R_1} = \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = 10$$

17) Parnatna vezava (negativna)


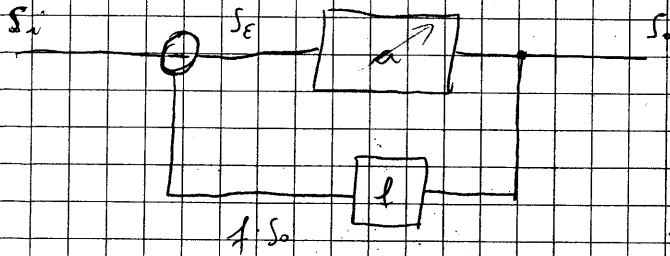


$$I_E = I_i - I_f$$

$$I_o = a I_E = a(I_i - I_f)$$

$$I_o(1 + a I_f) = a I_i$$

$$\frac{I_o}{I_i} = \frac{a}{1 + a I_f} \Big|_{a I_f \gg 1} = \frac{1}{I_f}$$

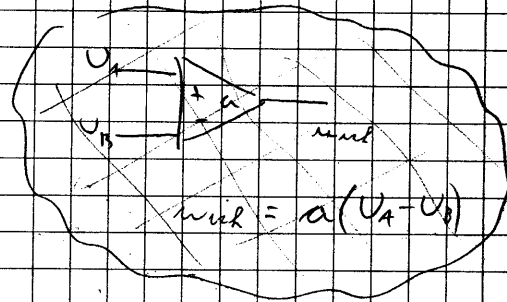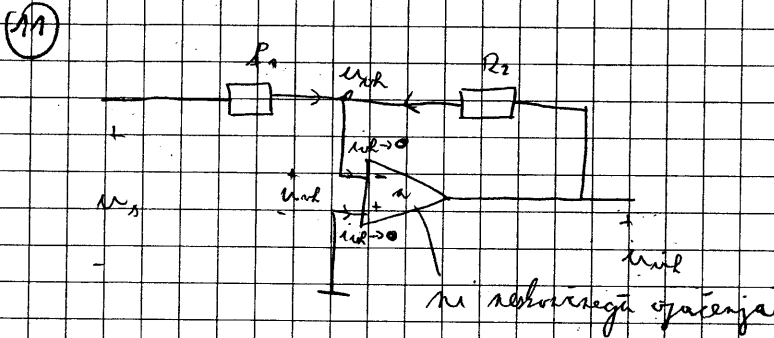

$$\frac{U_i - U_{in}}{R_1} + \frac{U_{in} - U_o}{R_2} = 0$$

$$\frac{U_i}{R_1} + \frac{U_{in}}{R_2} = U_o \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{U_i}{R_1} + \frac{U_o}{a} = U_o \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{U_o}{a} = \frac{U_o}{a} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{U_o}{R_2}$$

$$U_{in} = a U_o \Rightarrow U_o = \frac{U_{in}}{a}$$

$$A_u = \frac{U_o}{U_i}$$

$$\frac{U_o}{U_i} = \frac{R_2}{R_1} \frac{1}{1 + \frac{1}{a} \left(1 + \frac{R_2}{R_1} \right)} \Big|_{a \gg 1}$$


2 primera: $a = 10^3$, $a = 10^5$

$R_1 = 1 \text{ k}\Omega$

$R_2 = 10 \text{ k}\Omega$

1) $a = 10^3$: $A_u = \frac{10}{1} \cdot \frac{1}{1 + \frac{1}{10} \cdot (1 + 10)} = 10 \frac{1}{1 + \frac{11}{10}} = \underline{\underline{9,99}}$

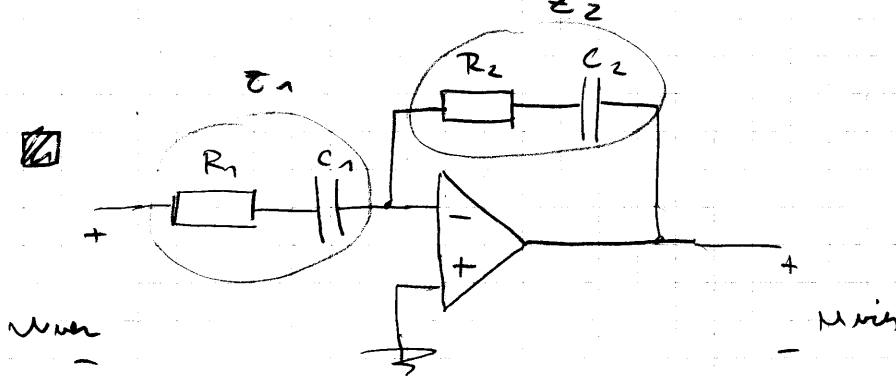2) $a = 10^5$: $A_u = \frac{10}{1} \cdot \frac{1}{1 + \frac{1}{10^5} \cdot (1 + 10)} = \underline{\underline{9999}}$



$R_1 = 1k\Omega$
 $R_2 = 10k\Omega$
 $C_1 = 1\mu F$
 $C_2 = 100nF$
 $A_u = \frac{u_{out}}{u_{in}} = ?$

$$A_u = -\frac{Z_2}{Z_1} = -\frac{R_2 + \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = -\frac{j\omega C_2 R_2 + 1}{j\omega C_2} \cdot \frac{j\omega C_1}{j\omega C_1 R_1 + 1} =$$


$$= -\frac{1 + j\omega C_2 R_2}{1 + j\omega R_1 C_1} \cdot \frac{j\omega C_1}{j\omega C_2} = -\frac{C_1}{C_2} \cdot \frac{1 + j\omega R_2 C_2}{1 + \frac{j\omega}{R_1 C_1}}$$


$$-\frac{C_1}{C_2} = -\frac{1\mu F}{100nF} = -0,01$$

$$\omega_{m1} = \frac{1}{R_2 C_2} = \frac{1}{10 \cdot 10^3 \cdot 10^{-7}} = 10^3$$

$$\omega_{m2} = \frac{1}{R_1 C_1} = \frac{1}{10^3 \cdot 10^{-6}} = 10^6$$
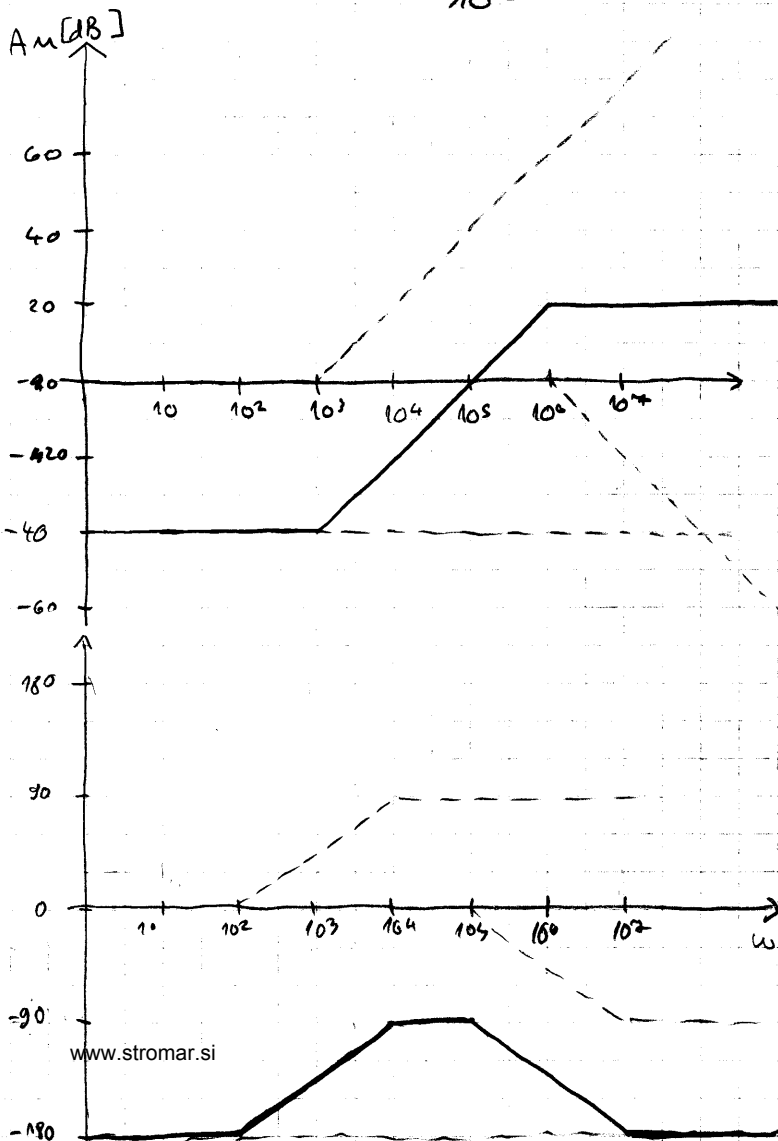
$$A_u = -10^{-2} \frac{1 + \frac{j\omega}{10^3}}{1 + \frac{j\omega}{10^6}}$$



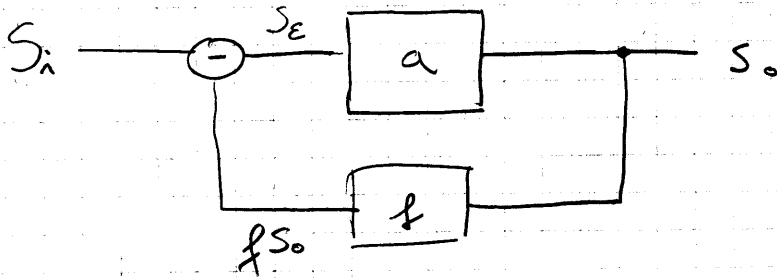


$$S_E = S_i - f S_o$$

$$S_o = a \cdot S_E \\ = a(S_i - f S_o)$$

$$S_o(1 + a f) = a S_i$$
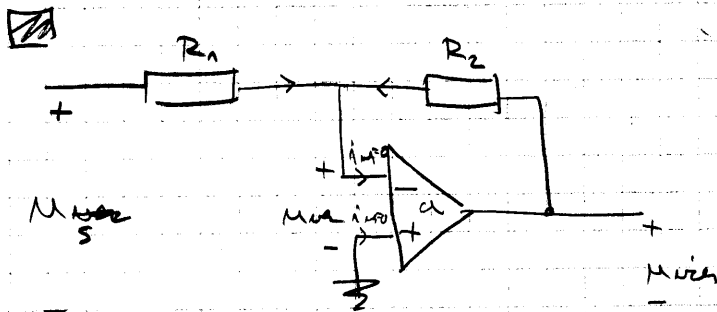
$$\frac{S_o}{S_i} = \frac{a}{1 + a f} \approx \frac{a}{a f} = \frac{1}{f}$$



$$U_{vch} = -a U_{ver}$$

$$U_{ver} = -\frac{U_{vch}}{a}$$

$$\frac{U_s - U_{ver}}{R_1} + \frac{U_{vch} - U_{ver}}{R_2} = 0$$

$$\frac{U_s}{R_1} + \frac{U_{vch}}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) U_{ver}$$

$$\frac{U_s}{R_1} + \frac{U_{vch}}{R_2} = -\frac{U_{vch}}{a} \left(\frac{1}{R_1} + \frac{1}{R_2}\right)$$

$$\frac{U_s}{R_1} = -\frac{U_{vch}}{a} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) - \frac{U_{vch}}{R_2}$$

$$\frac{U_{vch}}{U_s} = -\frac{R_2}{R_1} \frac{1}{1 + \frac{1}{a} \left(1 + \frac{R_2}{R_1}\right)} = -\frac{R_2}{R_1} \Big|_{a \gg 1}$$

$$a = 10^4, 10^5$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 10 \text{ k}\Omega$$


$$1) a = 10^4 :$$

$$A_u = - \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} \frac{1}{1 + \frac{1}{10^4} \left(1 + \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega}\right)} = -9,989$$

$$2) a = 10^5 :$$

$$A_u = - \frac{10}{1} \cdot \frac{1}{1 + \frac{1}{10^5} (1 + 10)} = -9,998$$

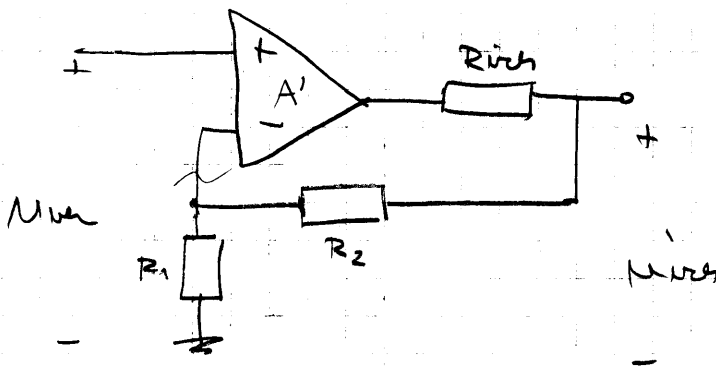■ Za podanu vezje dobite frekv. podelu
ajacanjji



$$A' = \frac{A_0}{1 + \frac{j\omega}{\omega_0}}$$

$$A_0 = 10^5$$


$$\omega_0 = 20\pi \cdot 10^{-1}$$

$$R_{vch} = 50 \Omega$$

$$R_1 = 10 \Omega$$

$$R_2 = 100 \Omega$$
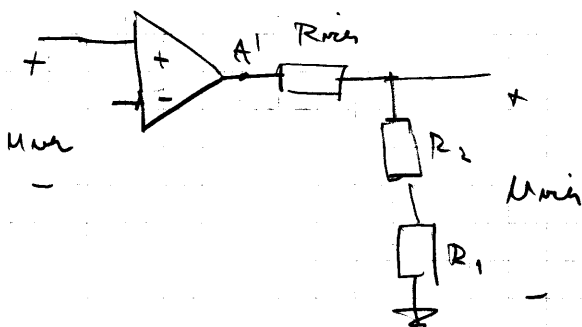
$$A_u = \frac{U_{vch}}{U_{vch}} = \frac{a}{1 + \frac{a}{10}}$$



$$U_{vch} = A' U_{vch} \frac{R_1 + R_2}{R_1 + R_2 + R_{vch}}$$

$$a = A' \frac{R_1 + R_2}{R_1 + R_2 + R_{vch}}$$

$$f = \frac{R_1}{R_1 + R_2} \left(U_{vch} = \frac{R_1}{R_1 + R_2} U_{vch} \right)$$

$$a = \frac{A_0}{1 + \frac{j\omega}{\omega_0}} \frac{R_1 + R_2}{R_1 + R_2 + R_{vch}} = 10^5 \frac{1}{1 + \frac{j\omega}{20\pi}} \cdot \frac{110}{160} = \frac{11}{16} \cdot \frac{10^5}{1 + \frac{j\omega}{20\pi}}$$

$$f = \frac{10}{110} = \frac{1}{11}$$


$$A_m = \frac{\frac{11}{16} \cdot 10^5 \frac{1}{1 + \frac{j\omega}{20\pi}}}{1 + \frac{1}{11} \cdot \frac{11}{16} \cdot 10^5 \frac{1}{1 + \frac{j\omega}{20\pi}}} =$$

$$= \frac{11 \cdot 10^5}{16 (1 + \frac{j\omega}{20\pi}) \left[1 + \frac{10^5}{16} \frac{1}{1 + \frac{j\omega}{20\pi}} \right]} =$$

$$= \frac{11}{16} \frac{10^5}{(1 + \frac{j\omega}{20\pi}) \frac{1 + \frac{j\omega}{20\pi} + \frac{10^5}{16}}{1 + \frac{j\omega}{20\pi}}} =$$

$$= \frac{11}{16} \cdot 10^5 \frac{1}{625 \cdot 1 + \frac{j\omega}{20\pi}} = \frac{11}{16} \frac{10^5}{625} \frac{1}{1 + \frac{j\omega}{20\pi \cdot 625}}$$

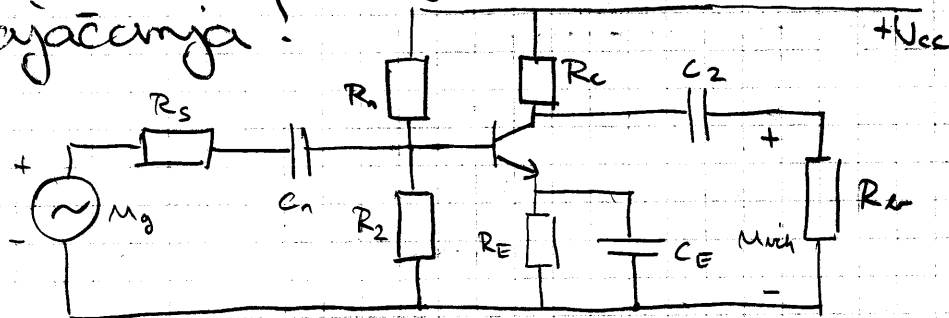Za podani ojač. delovite frekv. poteh 4.1. ojačanja!



- $R_s = 1 \text{ k}\Omega$
- $R_1 = 50 \text{ k}\Omega$
- $R_2 = 25 \text{ k}\Omega$
- $R_E = 5 \text{ k}\Omega$
- $R_C = 5 \text{ k}\Omega$
- $R_L = 2 \text{ k}\Omega$

$$U_{cc} = 12 \text{ V}$$


$$\beta = 100$$

$$r_{be} = 50 \Omega, C_{\pi} = 18 \text{ nF}, C_{\mu} = 2 \text{ pF}$$

$$C_1 = 3 \mu\text{F}, C_2 = 8 \mu\text{F}$$

$$C_E = 50 \mu\text{F}$$


$$A_m = \frac{u_{nch}}{u_g}$$

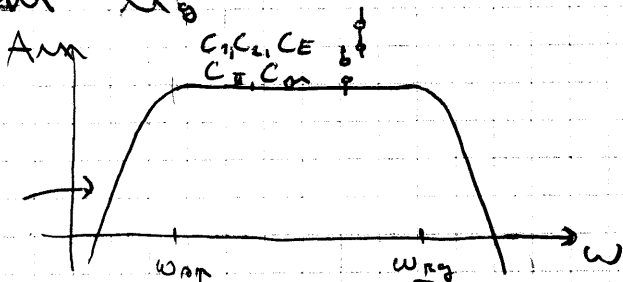


upliv C_1, C_2, C_E
 C_{π}, C_{μ}

upliv C_{π}, C_{μ}
 $C_1, C_2, C_E \rightarrow$

$$D.T.: I_C, U_{CE}$$

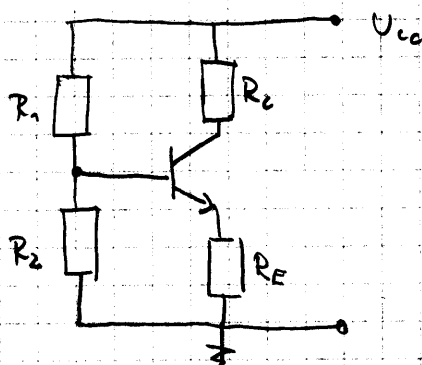

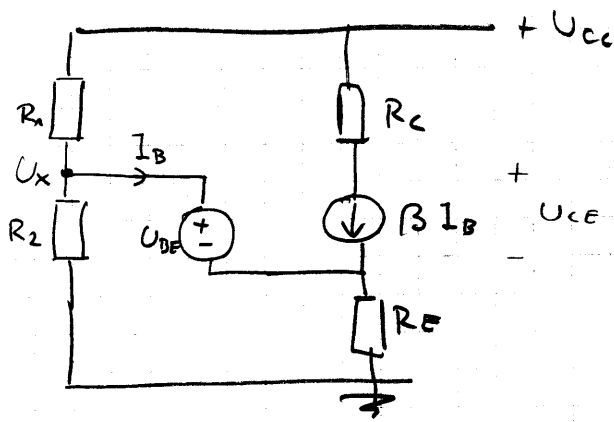

$$\frac{U_{cc} - U_x}{R_1} = \frac{U_x}{R_2} + I_B$$

$$U_x = U_{RE} + U_{BE} = (1 + \beta) I_B R_E + U_{BE}$$

$$\frac{U_{cc}}{R_1} = U_x \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + I_B$$

$$\frac{U_{cc}}{R_1} = U_x \frac{R_1 + R_2}{R_1 R_2} + I_B$$

$$\frac{U_{cc}}{R_1} = \frac{U_x}{R_1 \parallel R_2} + I_B$$

$$\frac{U_{cc}}{R_1} = \frac{(1 + \beta) R_E I_B + U_{BE}}{R_1 \parallel R_2} + I_B$$

$$\frac{U_{cc}}{R_1} = I_B \left[\frac{(1 + \beta) R_E}{R_1 \parallel R_2} + 1 \right] + \frac{U_{BE}}{R_1 \parallel R_2}$$

$$I_B = \frac{\frac{U_{cc}}{R_1} - \frac{U_{BE}}{R_1 \parallel R_2}}{\frac{(1 + \beta) R_E}{R_1 \parallel R_2} + 1}$$


$$I_C = \beta I_B = 0,633 \text{ mA}$$

$$g_m = \frac{I_C}{U_T} = 25,3 \text{ mS}, \quad r_{\pi} = \frac{\beta}{g_m} = 3,95 \text{ k}\Omega$$


$$U_{ce} = U_{cc} - I_C (R_C + R_E) = 12 - 0,633 \text{ mA} \cdot 10 \text{ k}\Omega = 5,67 \text{ V}$$

Sp. frekv. meja:

1) uticaj C_1 :

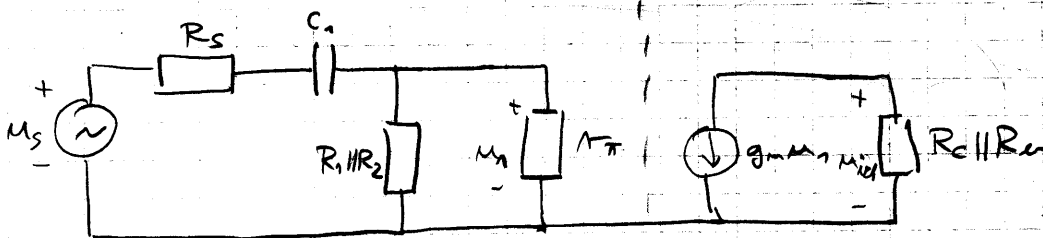

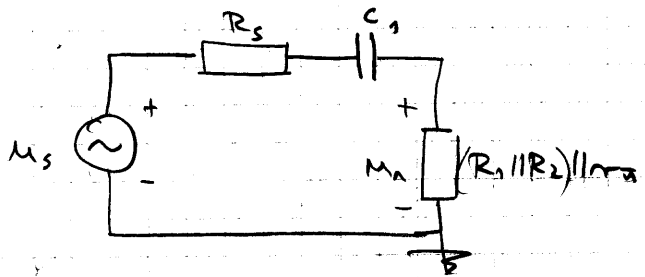Dovolj, da dobimo $u_1 = f(u_s)$, v u res je mestikava itak neodvisna od frekv.




$$u_n = \frac{(R_1 \parallel R_2) \parallel r_{\pi}}{R_s + (R_1 \parallel R_2) \parallel r_{\pi} + \frac{1}{j\omega C_1}} \cdot u_s =$$

$$H(j\omega) = \frac{(R_1 \parallel R_2) \parallel r_{\pi} \cdot j\omega C_1}{1 + [(R_1 \parallel R_2) \parallel r_{\pi} + R_s] j\omega C_1}$$

$$K = (R_1 \parallel R_2) \parallel r_{\pi} \cdot C_1$$

$$\omega_{RC_1} = \frac{1}{[(R_1 \parallel R_2) \parallel r_{\pi} + R_s] C_1} = \underline{79,5 \text{ s}^{-1}}$$

2) upliv C_2

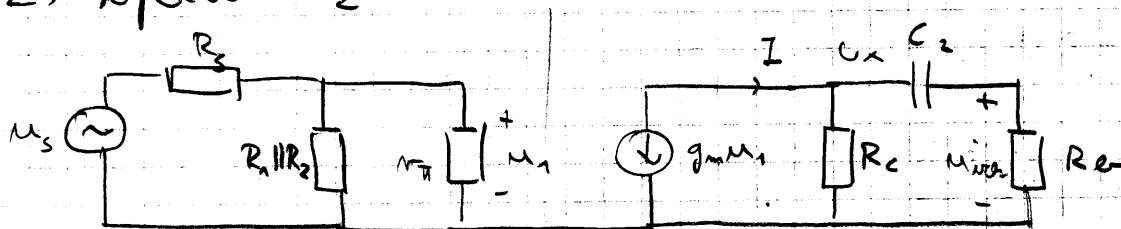

Spet nas lahko zanima le $u_{\text{vich}}(u_n) = f(u_n)$ - samo ta frekv. odvisen

$$I = -g_m u_n = \frac{U_x}{R_c} + \frac{U_x}{R_w + \frac{1}{j\omega C_2}} = U_x \left(\frac{1}{R_c} + \frac{j\omega C_2}{1 + j\omega C_2 R_w} \right) =$$

$$= U_x \frac{1 + j\omega C_2 R_w + j\omega C_2 R_c}{R_c (1 + j\omega C_2 R_w)} = U_x \frac{1 + j\omega C_2 (R_w + R_c)}{R_c (1 + j\omega C_2 R_w)}$$

$$U_x = I \frac{R_c (1 + j\omega C_2 R_w)}{1 + j\omega C_2 (R_w + R_c)}$$


$$u_{\text{vich}} = \frac{R_w}{R_w + \frac{1}{j\omega C_2}} U_x = \frac{R_w j\omega C_2}{(1 + R_w j\omega C_2)} \frac{(1 + j\omega C_2 R_w) R_c}{1 + j\omega C_2 (R_w + R_c)} \cdot I$$

$$u_{\text{vich}} = -g_m \frac{j\omega C_2 R_w R_c}{1 + j\omega C_2 (R_w + R_c)} u_n$$

$$K = -g_m C_2 R_w R_c$$

$$\omega_{RC_2} = \frac{1}{C_2 (R_w + R_c)} = \underline{17,86 \text{ s}^{-1}}$$

3) vpliv C_E Z_o

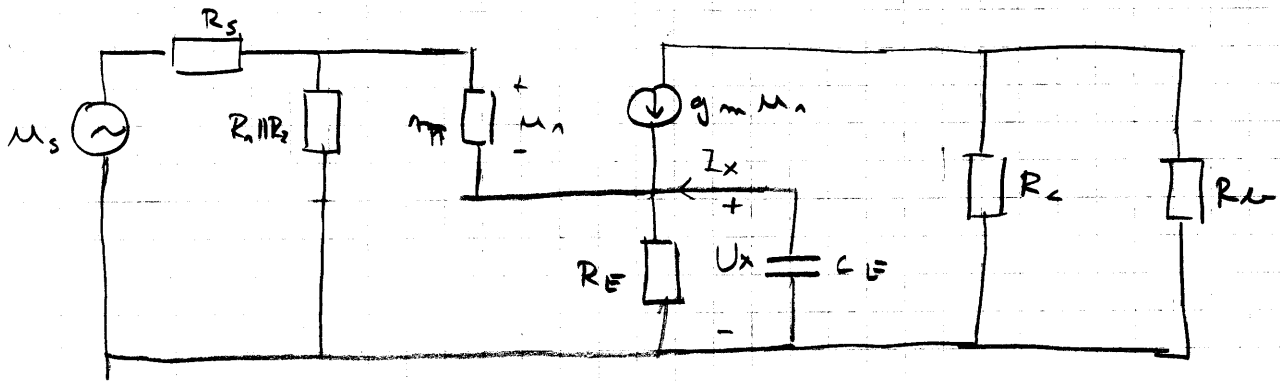

$R_{EKV} = \frac{U_x}{I_x}$ - iz pr. primerov vidimo, da $\omega_T = \frac{1}{C \cdot R_{EKV}}$


$I_x = \frac{U_x}{R_E} + \frac{U_x}{r_{\pi} + (R_1 || R_2) || R_s} + \frac{g_m r_{\pi}}{r_{\pi} + (R_1 || R_2) || R_s} U_x$

$= U_x \left[\frac{1}{R_E} + \frac{1 + g_m r_{\pi}}{r_{\pi} + (R_1 || R_2) || R_s} \right]$



$\frac{U_x}{I_x} = R_{EKV} = \frac{1}{\frac{1}{R_E} + \frac{1 + g_m r_{\pi}}{r_{\pi} + (R_1 || R_2) || R_s}} = 48 \Omega$

$\omega_{p3} = \frac{1}{C_E \cdot R_{EKV}} = 416 \text{ rad}^{-1}$


Sp. frekv. meja doloca ω_{p3}

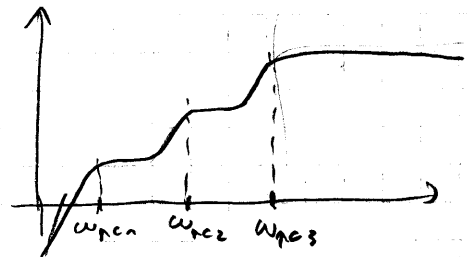

Zg. frekv. meja:

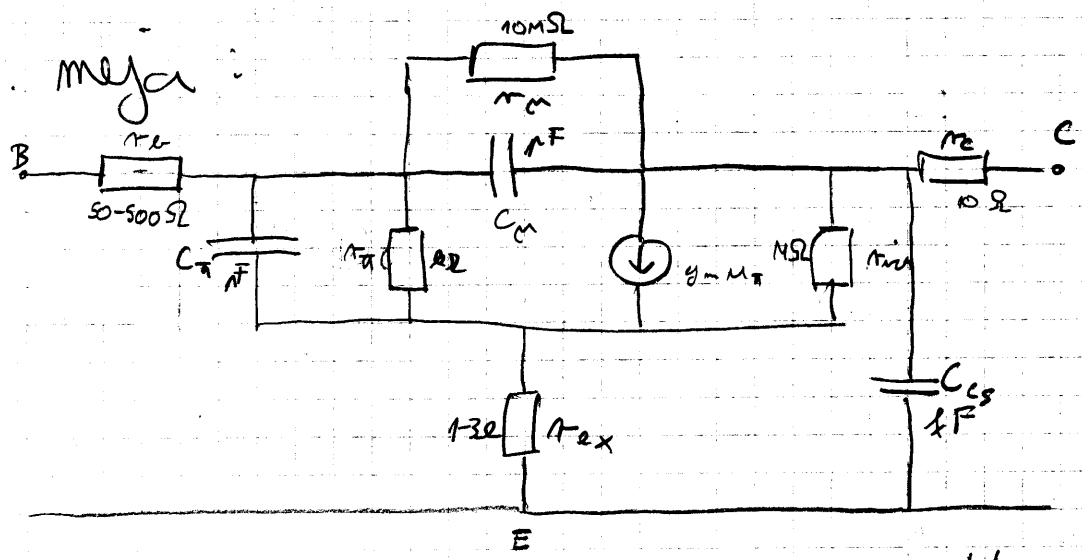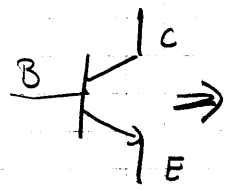

Poenostavljena vezava:

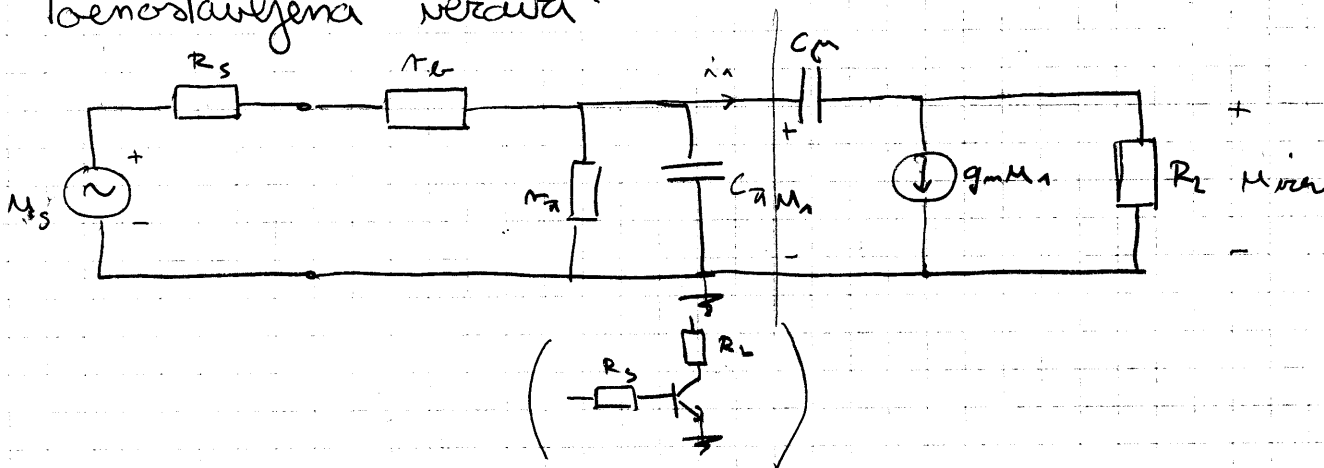

$$i_1 = (u_1 - u_{vch}) j\omega C_\mu$$

$$g_m u_1 + u_{vch} \cdot \frac{1}{R_L} + (u_{vch} - u_1) j\omega C_\mu = 0$$



$$g_m u_1 = - \frac{u_{vch}}{R_L}$$


$$u_{vch} = - g_m R_L u_1$$

$$i_1 = (u_1 - u_{vch}) j\omega C_\mu = (u_1 - (-g_m R_L u_1)) j\omega C_\mu$$

$$i_1 = u_1 (1 + g_m R_L) j\omega C_\mu$$

$$\frac{i_1}{u_1} = (1 + g_m R_L) j\omega C_\mu = \underbrace{C_{\mu n}}_{|A_n|} j\omega C_\mu$$

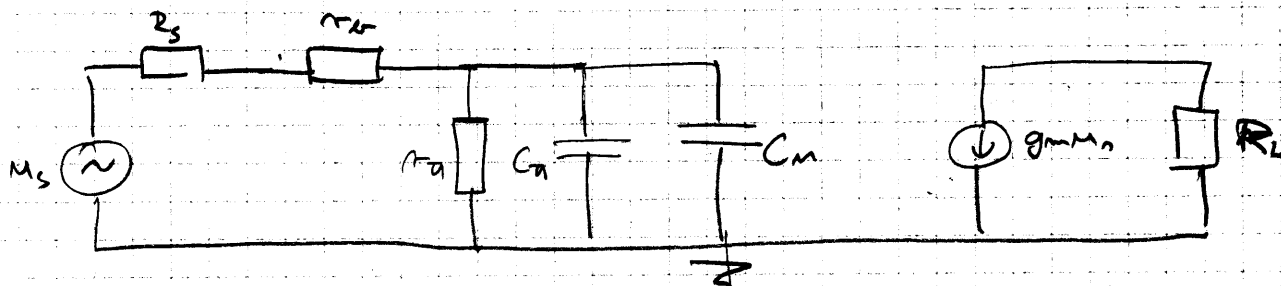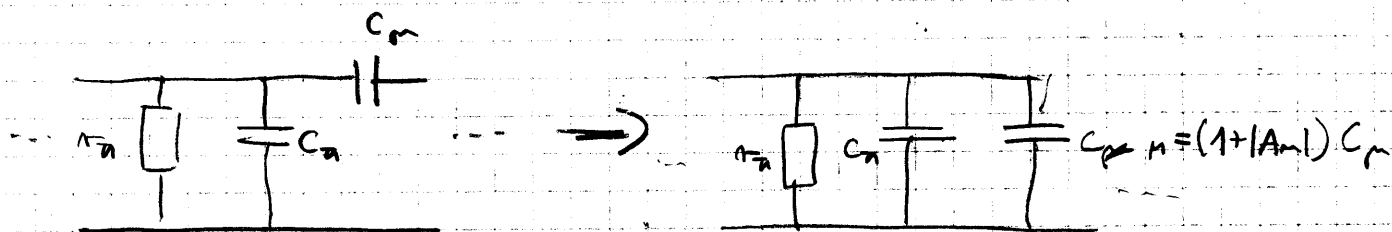

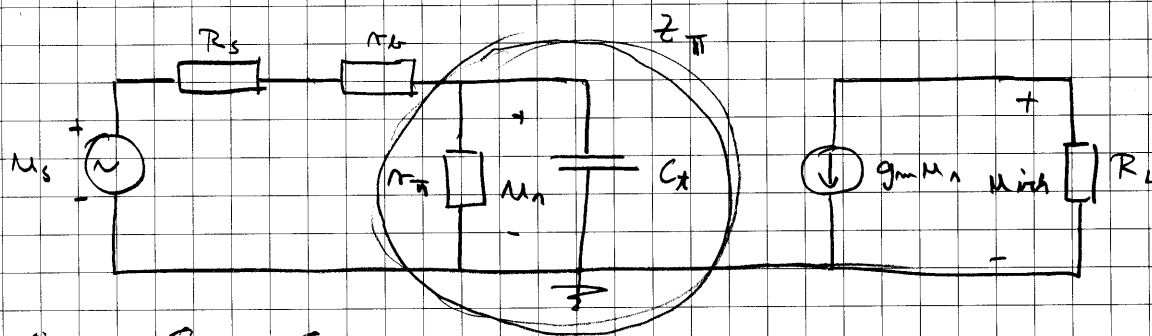

$$C_t = C_{\pi} + C_m$$

$$A_m = \frac{u_{vch}}{u_s}$$

$$Y_{\pi} = \frac{1}{r_{\pi}} + j\omega C_t = \frac{1 + j\omega C_t r_{\pi}}{r_{\pi}}$$

$$Z_{\pi} = \frac{r_{\pi}}{1 + j\omega C_t r_{\pi}}$$

$$u_{vch} = -g_m u_n R_L$$

$$u_n = \frac{Z_{\pi}}{Z_{\pi} + R_s + r_{be}} u_s$$

$$u_{vch} = -g_m R_L \frac{Z_{\pi}}{Z_{\pi} + R_s + r_{be}} u_s$$

$$A_m = -g_m R_L \frac{Z_{\pi}}{Z_{\pi} + R_s + r_{be}}$$



$$A_m = -g_m R_L \frac{\frac{r_{\pi}}{1 + j\omega C_t r_{\pi}}}{\frac{r_{\pi}}{1 + j\omega C_t r_{\pi}} + R_s + r_{be}} =$$

$$= -g_m R_L \frac{r_{\pi}}{r_{\pi} + j\omega C_t r_{\pi} (R_s + r_{be}) + R_s + r_{be}} =$$

$$\frac{-g_m R_L r_{\pi}}{(1 + j\omega C_t r_{\pi})(R_s + r_{be})}$$

$$= -\frac{g_m R_L r_{\pi}}{r_{\pi} + R_s + r_{be}} \frac{1}{1 + j\omega \frac{C_t r_{\pi} (R_s + r_{be})}{r_{\pi} + R_s + r_{be}}}$$
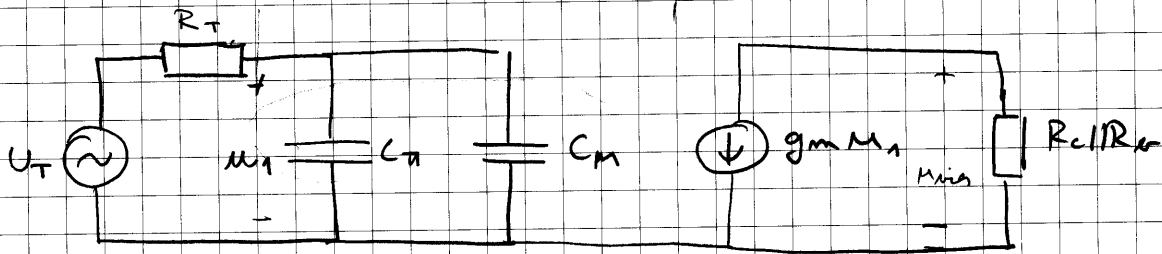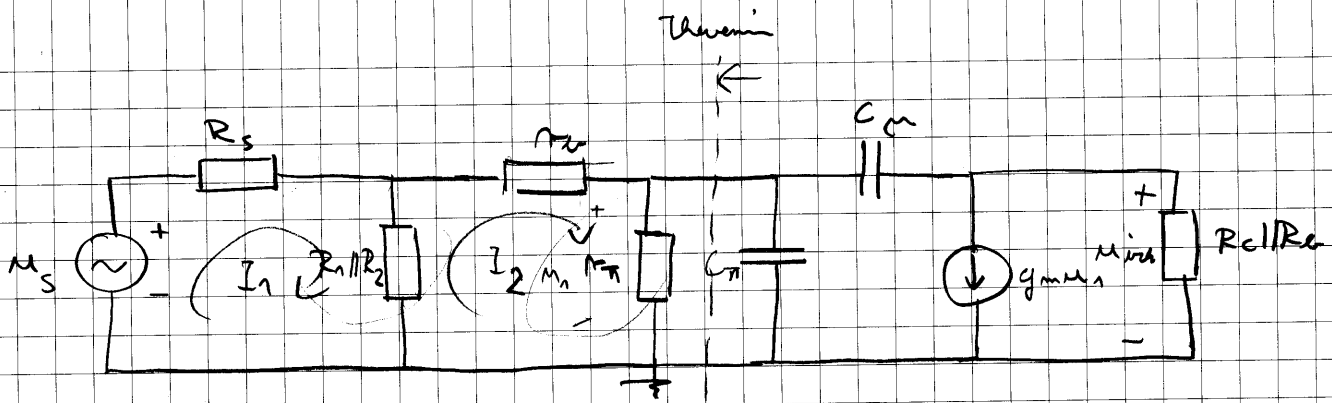
$$\omega_p = \frac{r_{\pi} + R_s + r_{be}}{C_t r_{\pi} (R_s + r_{be})}$$



$$U_s = I_1 (R_s + R_1 || R_2) - I_2 (R_1 || R_2)$$

$$0 = -I_1 (R_1 || R_2) + I_2 (R_1 || R_2 + r_{out} + r_{\pi})$$

$$I_1 = \frac{I_2 (R_1 || R_2 + r_{out} + r_{\pi})}{R_1 || R_2}$$

$$U_s = \frac{I_2 (R_1 || R_2 + r_{out} + r_{\pi}) (R_s + R_1 || R_2) - I_2 R_1 || R_2}{R_1 || R_2}$$

$$I_2 = \frac{U_s \cdot R_1 || R_2}{R_s (R_1 || R_2 + r_{out} + r_{\pi}) + R_1 || R_2 (r_{out} + r_{\pi})}$$


$$U_T = I_2 r_{\pi} = \frac{U_s \cdot R_1 || R_2 \cdot r_{\pi}}{R_s (R_1 || R_2 + r_{out} + r_{\pi}) + R_1 || R_2 (r_{out} + r_{\pi})}$$

$$R_T = (R_s || (R_1 || R_2) + r_{out}) || r_{\pi}$$

$$C_m = (1 + |A_{v1}|) C_\pi$$

$$|A_{v1}| = g_m R_c || R_L$$

$$C_T = C_{\pi} + C_{m1}$$

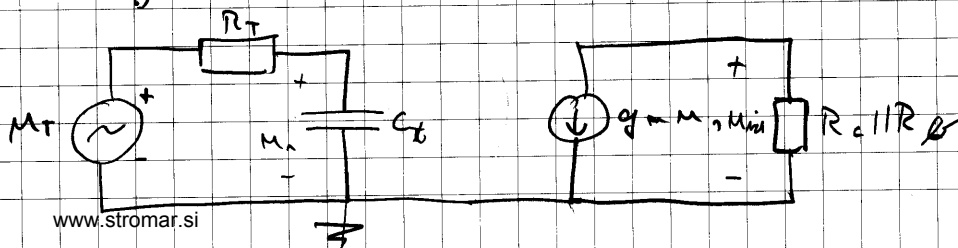

$$A_m = \frac{u_{\text{rich}}}{u_s} = \frac{u_{\text{rich}}}{u_T} \cdot \frac{u_T}{u_s}$$

$$u_{\text{rich}} = -g_m u_n R_c \parallel R_L$$

$$u_n = \frac{\frac{1}{j\omega C_T}}{\frac{1}{j\omega C_T} + R_T} u_T = \frac{1}{1 + j\omega C_T R_T} u_T$$

$$u_{\text{rich}} = -g_m R_c \parallel R_L \frac{1}{1 + j\omega C_T R_T} u_T$$

$$\frac{u_{\text{rich}}}{u_T} = - \frac{g_m R_c \parallel R_L}{1 + j\omega C_T R_T} = K \frac{1}{1 + \frac{j\omega}{\omega_n}}$$

$$K = -g_m R_c \parallel R_L$$

$$\omega_n = \frac{1}{C_T R_T}$$

$$A_m = -g_m R_c \parallel R_L \frac{R_1 \parallel R_2 \cdot u_T}{R_s (R_1 \parallel R_2 + r_b + r_{\pi}) + R_1 \parallel R_2 (r_b + r_{\pi})} \frac{1}{1 + \frac{j\omega}{\frac{1}{C_T R_T}}}$$

$$\omega_n = \frac{1}{(C_n + C_m) R_T} = \frac{1}{(C_n + (1 + g_m R_c \parallel R_L) C_m) [(R_s \parallel (R_1 \parallel R_2) + r_b) \parallel r_{\pi}]}$$

$$K = -27,27$$

$$\omega_n = 1,36 \cdot 10^7 \text{ s}^{-1}$$

