

3. 34 AM dos. dr. a) $\eta_N = \frac{P_N}{\sqrt{3} U_1 I_{1N} \cos \varphi_{1N}} = \frac{5500 \text{ W}}{\sqrt{3} \cdot 380 \text{ V} \cdot 13 \text{ A} \cdot 0,76} = 0,85$

$P_N = 5,5 \text{ kW}$

$U_1 = 380 \text{ V}$

$f_1 = 50 \text{ Hz}$

$I_{1N} = 13 \text{ A}$

$\cos \varphi_{1N} = 0,76$


$n_N = 945 \text{ min}^{-1}$

$E_{20} = 158 \text{ V}$

$I_{20} = 21,3 \text{ A}$

$M_0 / M_N = 3$

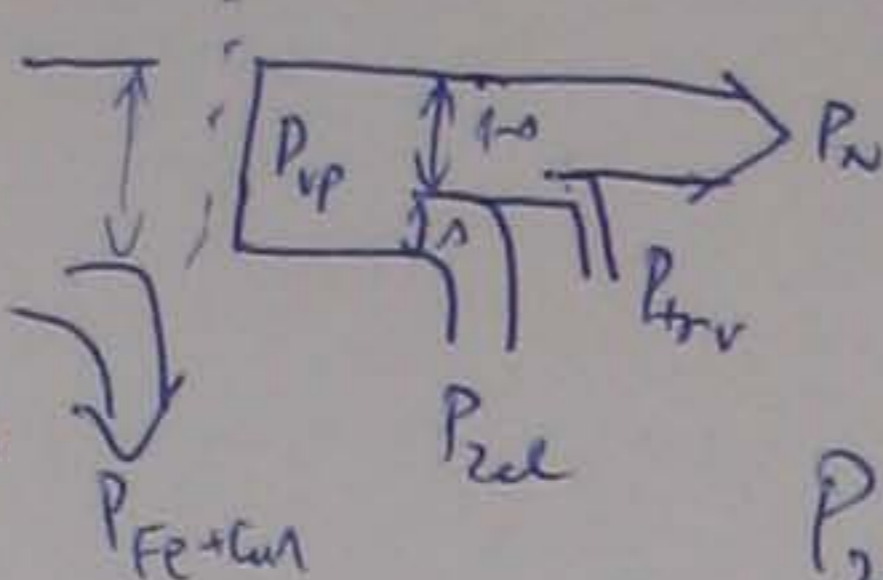$M_s = \frac{60 \text{ A}}{p} (\text{max. v\u011bj}) = \frac{300}{3} = 1000 \text{ min}^{-1}$
 $\Delta_N = \frac{M_s - n_N}{M_s} = \frac{1000 - 945}{1000} = 0,055$



$P_{\text{mech}} = \frac{P_{\text{up}}}{1 - \Delta_N}$
 $P_N + P_{\text{ruv}} = P_{\text{up}} (1 - \Delta_N)$
 $P_{\text{up}} = \frac{P_N + P_{\text{ruv}}}{1 - \Delta_N} = \frac{5500 + 100}{1 - 0,055} \text{ W} = 5926 \text{ W}$

$P_{\text{rel}} = \Delta P_{\text{up}} = 0,055 \cdot 5926 \text{ W} \approx 326 \text{ W}$

$P_{\text{Fe+Cui}} + P_{\text{ruv}} = P_{1N} - P_{\text{up}} = \sqrt{3} U_1 I_{1N} \cos \varphi_{1N} - P_{\text{up}} = 577 \text{ W}$

$E_2 = s E_{20} = 0,055 \cdot 158 \text{ V} = 8,69 \text{ V}$
 $f_2 = s f_1 = 2,75 \text{ Hz}$

b) $M_N = \frac{2 M_{\text{om}}}{\Delta_N + \frac{\Delta_{\text{om}}}{\Delta_N}}$ $x = \frac{\Delta_{\text{om}}}{\Delta_N}$
 $a = \frac{n_N}{M_N}$ $x^2 - 2ax + 1 = 0$

a) $M_{\text{ruv}} = 1000 \text{ W}$
 $M_{\text{om}} = M_s (1 - \Delta_{\text{om}}) = M_s (1 - x \Delta_N) = 1000 \text{ min}^{-1} (1 - 5,8 \dots \cdot 0,055) = 679$
 $x_{1,2} = a \pm \sqrt{a^2 - 1} = 3 \pm \sqrt{3^2 - 1} = 0,17 \dots$
 $= 5,828 \dots$ ($\Delta_{\text{om}} > \Delta_N$)

$P = M_N \omega_N$ $M_N = \frac{P_N}{\omega_N} = \frac{P_N \cdot 60}{2\pi n_N} = \frac{5500 \cdot 60}{2\pi \cdot 945} = 55,57 \dots \text{ Nm}$

$M_{\text{om}} = 3 \cdot M_N = 167 \text{ Nm}$

c) $M', P'_2, E'_2, f'_2, P'_{\text{rel}}$

$R_{\text{red}} = 3,2 \Omega$ $R_2 = \frac{s E_{20} \text{ konst.}}{\sqrt{3} I_2}$ $R_{2N} = \frac{\Delta_N E_{20}}{\sqrt{3} I_{2N}} = \frac{0,055 \cdot 158 \text{ V}}{\sqrt{3} \cdot 21,3 \text{ A}} = 0,2355 \Omega$
 $R_2 = R_{2N} + R_{\text{red}} = 3,2355 \dots \Omega$

$\Delta' = \frac{R_2 \sqrt{3} I_{2N}}{E_{20}} = \frac{\sqrt{3} \cdot 21,3 \text{ A} \cdot 3,2355 \Omega}{158 \text{ V}} = 0,75548 \dots$ $n' = M_s (1 - \Delta') = 245 \text{ min}^{-1}$

$E'_2 = s' E_{20} = 119 \text{ V}$ $f'_2 = s' f_1 = 38 \text{ Hz}$ PREDPOSTAVKA $M = M_N$

$P'_2 = P_N \cdot \frac{n'}{M_N} = 5500 \text{ W} \cdot \frac{245}{945} = 1426 \text{ W}$

$P_{\text{rel}} = \frac{\Delta'}{1 - \Delta'} (P'_2 + P_{\text{ruv}}) = \frac{0,755 \dots}{1 - 0,755 \dots} (1426 \text{ W} + 100 \text{ W}) = 4714 \text{ W}$

4. EM TUSE

$M_b = \text{konst.}$

$P_N = 25 \text{ kW}$

$U_N = 220 \text{ V}$

$n_N = 600 \text{ min}^{-1}$

$I_N = 132 \text{ A}$


$R_{sc} = 0,416 \Omega$

$\Delta U_{sc} = 2 \text{ V}$

a) $R_d = 0,35 \Omega$

mar. vrb. $n' = ?$

$U' = \frac{U_N}{2}$

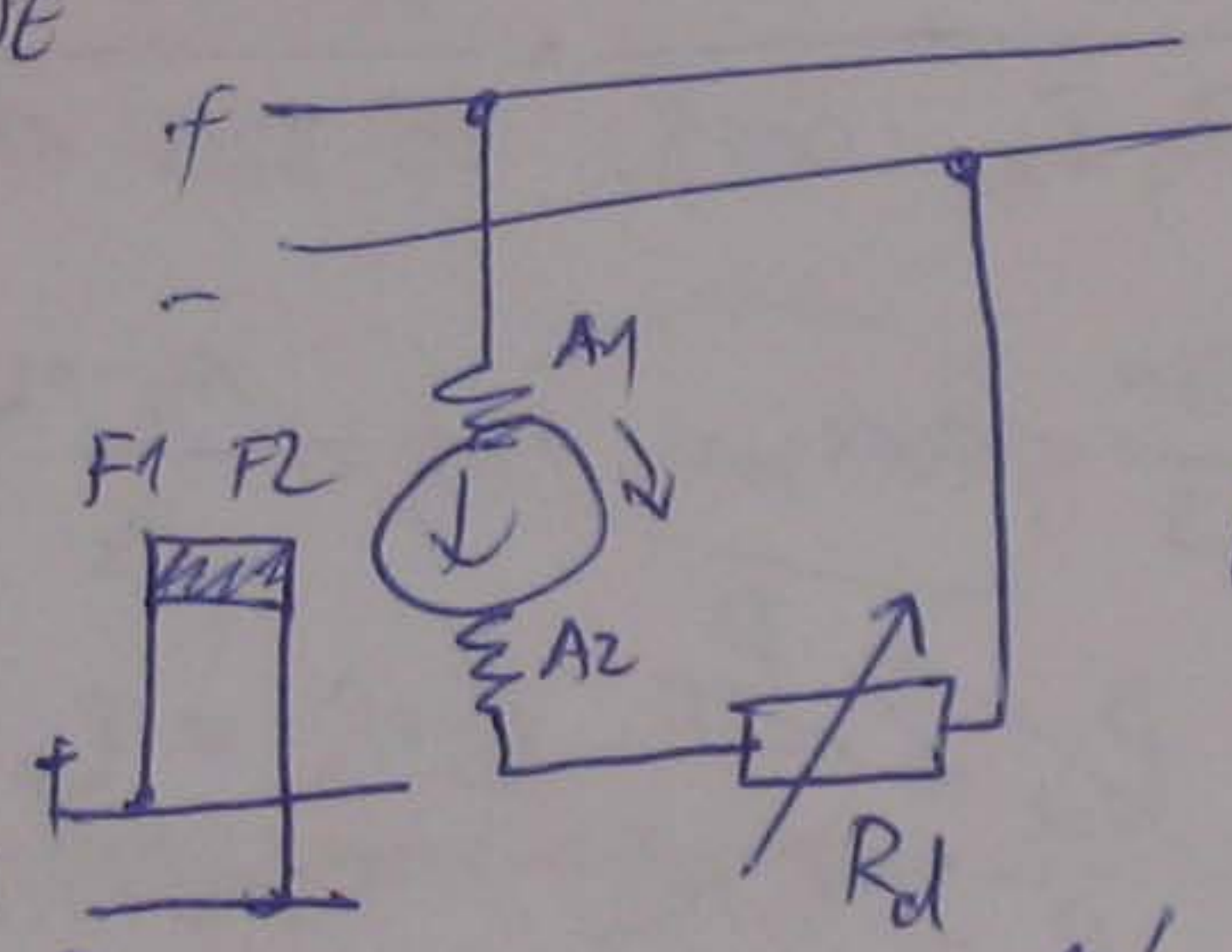


$\Phi = k_\phi I_v$

$E = k_e \cdot n \cdot \Phi = k_e k_\phi m \bar{I}_v$

$M = k_{em} \cdot \bar{I}_i \Phi = k_{em} k_\phi I_v \bar{I}_i$


$E \propto n$ $\frac{n'}{n_N} = \frac{E'}{E_N} = \frac{0,5 U_N - (R_c + R_d) I_{in} - \Delta U_{sc}}{U_N - R_c I_{in} - \Delta U_{sc}}$

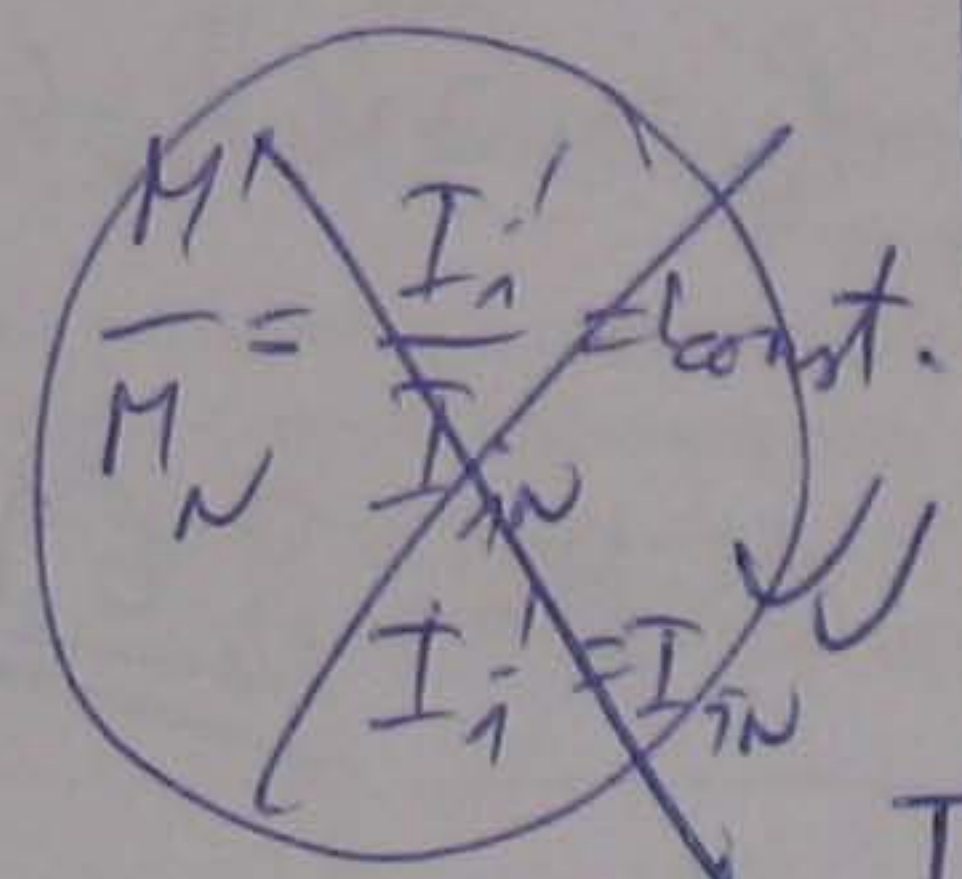$E = U - R_c I_i - \Delta U_{sc}$ $n' = n_N \cdot \frac{110 \text{ V} - (0,416 \Omega) \cdot 132 \text{ A} - 2 \text{ V}}{220 \text{ V} - 0,416 \Omega \cdot 132 \text{ A} - 2 \text{ V}}$



$= 157 \text{ min}^{-1}$

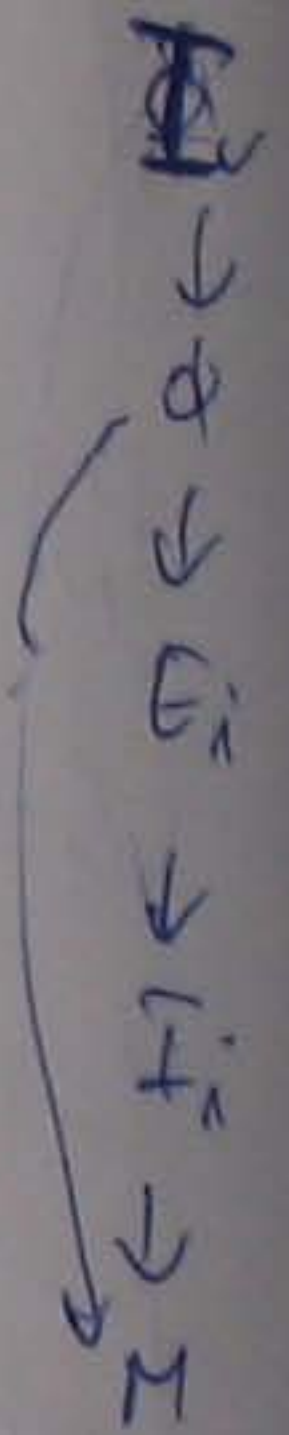~~$I_i' = \frac{U'}{R'} = \frac{U_N}{2(R_c + R_d)} = \frac{220 \text{ V}}{2(0,416 \Omega)}$~~



b)

$$U_N \quad \frac{E'}{E_N} = \frac{M' \phi'}{M_N \phi_N} = \frac{M' \cdot 0,6 \phi_N}{M_N \phi_N} = \frac{0,6 M'}{M_N} = \frac{U_N - R_c I_i' - s U_{3\%}}{U_N - E_N}$$

$$\phi' = 0,6 \phi_N$$

$$M', I_i' = ? \quad E_N = U_N - R_c I_{iN} - s U_{3\%} = \underline{\underline{202,688V}}$$

$$R_d \rightarrow M'' = ? \quad M = k_m I_i \phi$$

$$A = \frac{M'}{M_N} = \frac{k_m I_i' \phi' \cdot 0,6 \phi_N}{k_m I_{iN} \phi_N} = \frac{0,6 I_i'}{I_{iN}}$$

$$I_i' = I_{iN} \cdot \frac{1}{0,6} = \underline{\underline{220A}}$$

$$M' = \frac{M_N}{0,6} \cdot \frac{U_N - R_c I_i' - s U_{3\%}}{202,688V} = \frac{600}{0,6} \cdot \frac{220V - 0,165\Omega \cdot 220A - 2V}{202,688} =$$

$$= \underline{\underline{950 \text{ min}^{-1}}}$$

$$M'' = \frac{M_N}{0,6} \cdot \frac{U_N - (R_c + R_d) I_i' - s U_{3\%}}{E_N} = \frac{600}{0,6} \cdot \frac{220 - 0,416 \cdot 220 - 2}{202,688} = \underline{\underline{624 \text{ min}^{-1}}}$$